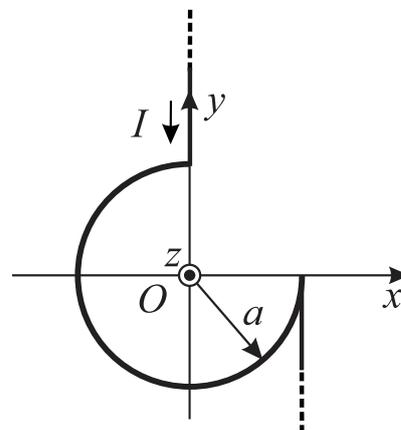


ZADACI

Zadatak 1. Veoma dugačak provodnik je savijen kao što je prikazano na slici 1. Celokupan sistem leži u x - y ravni pravouglog Dekartovog koordinatnog sistema. Odrediti intenzitet vektora magnetske indukcije u koordinatnom početku. Sredina je vazduh.

Brojne vrednosti su: $I = 10$ A, $a = 10$ cm, $\mu_0 = 4\pi \cdot 10^{-7}$ H/m.




Slika 1.


Zadatak Na slici 2 je prikazano debelo torusno jezgro, načinjeno od dva različita materijala i njihove krive prvobitnog magnetisanja. Na jezgro je ravnomerno namotano $N = 170$ zavojaka u kojima se uspostavila struja jačine I . Odrediti:

- jačinu struje, I , pri kojoj će tri četvrtine dela jezgra načinjenog od materijala 2 biti u zasićenju, i
- fluks vektora magnetske indukcije kroz poprečni presek jezgra, pri struji određenoj pod a).

Dimenzije jezgra su: $a = 3$ cm, $b = 5$ cm, $h_1 = h_2 = 1$ cm.

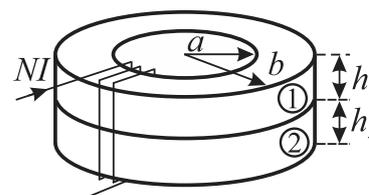

Slika 2a

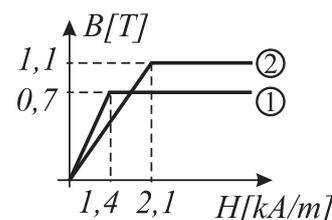

Slika 2b

PRAVILA POLAGANJA

Za položen kolokvijum neophodno je sakupiti više od 50% od ukupnog broja poena na zadacima. Svaki zadatak se boduje sa 25 poena. Kolokvijum traje jedan sat i trideset minuta.


ZADACI

Zadatak 1. Na slici 1a je prikazana mreža reaktivnih komponenti, a na slici 1b "fizička" šema dva magnetski spregnuta kalemna.


- Izračunati ekvivalentnu impedansu Z_{AB} mreže sa slike 1a, i odrediti sve rezonantne i antirezonantne učestanosti.
- Ako se kolo na slici 1a priključi između tačaka A i B na slici 1b i ako generator radi na manjoj rezonantnoj učestanosti, skicirati električnu šemu novog kola i postaviti odgovarajuće tačke, kojima se na ovoj šemi prikazuje smer namotavanja kalemova.
- Izračunati kompleksnu snagu strujnog generatora.

Brojne vrednosti su:

$$L = 20 \text{ mH}, M = 12 \text{ mH}, C = 5 \text{ nF}, C_1 = 2,5 \text{ nF}, I_S = (1-j1) \text{ mA}.$$

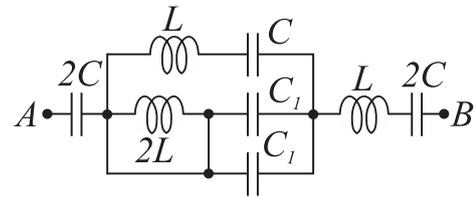

Slika 1a.

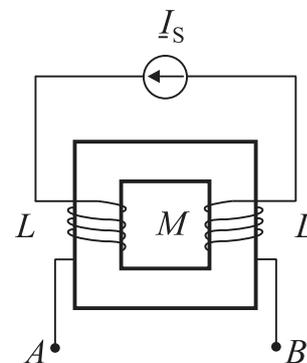


Slika 1b.

Zadatak 2. Simetričan trofazni prijemnik, sa slike 2, priključen je na mrežu faznog napona prve faze $U_1 = 230 \text{ V}$.

- Odrediti pokazivanja idealnih mernih instrumenata.
- Na istom fazorskom dijagramu prikazati fazore svih veličina od kojih zavise pokazivanja idealnih mernih instrumenata.

Brojni podaci: $R = 30 \Omega$, $X_L = 20 \Omega$.

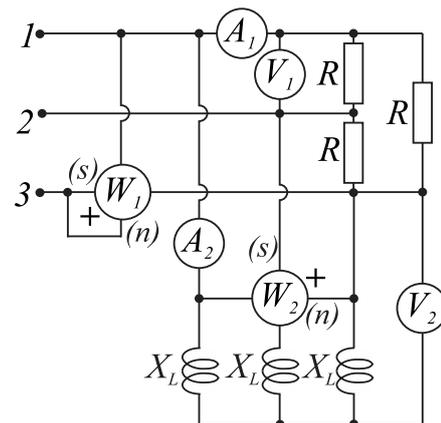


Slika 2.


PRAVILA POLAGANJA

Za položen kolokvijum neophodno je sakupiti više od 50% od ukupnog broja poena na zadacima. Svaki zadatak se boduje sa 25 poena. Kolokvijum traje jedan sat i trideset minuta.

K1 Z1

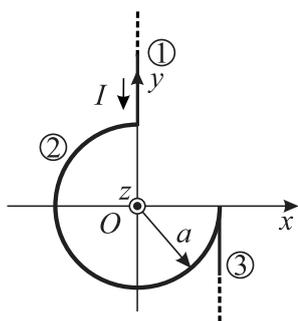
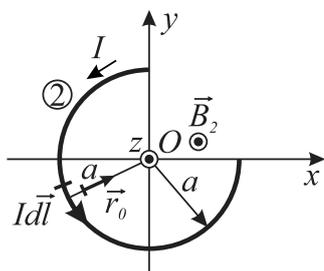
$$\boxed{\vec{B}_1 = 0} \quad (I \vec{dl} \times \vec{r}_0 = 0)$$




$$d\vec{B}_2 = \frac{\mu_0 I \vec{dl} \times \vec{r}_0}{4\pi r^2}$$

$$dB_2 = \frac{\mu_0 I dl}{4\pi a} \sin \sphericalangle(\vec{dl}, \vec{r}_0) = \frac{\mu_0 I dl}{4\pi a^2} \quad \sphericalangle(\vec{dl}, \vec{r}_0) = \frac{\pi}{2}$$

$$B_2 = \frac{\mu_0 I}{4\pi a^2} \int_0^{\frac{3}{2}\pi} dl = \frac{\mu_0 I}{4\pi a^2} \frac{3}{2} a\pi$$

$$\boxed{B_2 = \frac{3\mu_0 I}{8a}}$$
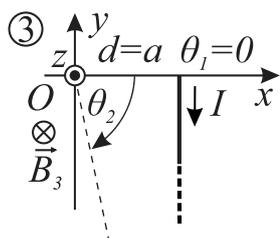
$$\boxed{\vec{B}_2 = B_2 \cdot \vec{i}_z}$$



$$\theta_1 = 0, \quad \theta_2 \rightarrow \frac{\pi}{2}, \quad d = a$$

$$B_3 = \frac{\mu_0 I}{4\pi d} (\sin \theta_2 - \sin \theta_1) = \frac{\mu_0 I}{4\pi a} \left(\sin \frac{\pi}{2} - \sin 0 \right) = \frac{\mu_0 I}{4\pi a} (1 - 0)$$


$$\boxed{B_3 = \frac{\mu_0 I}{4\pi a}}$$

$$\boxed{\vec{B}_3 = B_3 \cdot (-\vec{i}_z)}$$

$$\boxed{\vec{B}_0 = \vec{B}_1 + \vec{B}_2 + \vec{B}_3 = (B_2 - B_3) \cdot \vec{i}_z = \left(\frac{3\mu_0 I}{8a} - \frac{\mu_0 I}{4\pi a} \right) \cdot \vec{i}_z = \frac{\mu_0 I}{4a} \left(\frac{3}{2} - \frac{1}{\pi} \right) \cdot \vec{i}_z}$$

$$\boxed{\vec{B}_0 = 37,12 \mu\Gamma \cdot \vec{i}_z}$$

K1 Z2

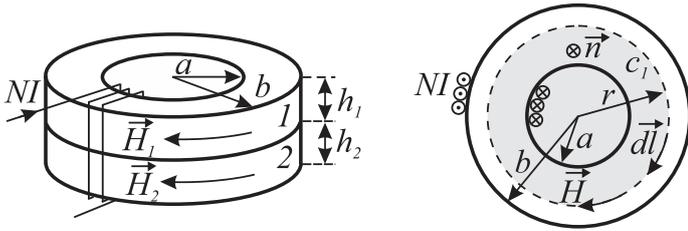

Granični uslov: $H_{1r} = H_{2t} = H$

$$\oint_c \vec{H} \cdot d\vec{l} = NI$$

$$H 2\pi r = NI$$

$$H = \frac{NI}{2\pi r} \quad a \leq r \leq b$$

a)

$$r_z = a + \frac{3}{4}(b-a) = 4,5 \text{ cm}$$



$$\frac{NI}{2\pi r_z} = H_{c2} = 2100 \text{ A/m} \quad \rightarrow \quad I = \frac{H_{c2} 2\pi r_z}{N} = \frac{2100 \cdot 2\pi \cdot 0,045}{170} \quad \boxed{I = 3,49 \text{ A}}$$

b)

$$H_{1\text{max}}(r=a) = \frac{NI}{2\pi a} = 3150 \text{ A/m}$$

$$H_{1\text{min}}(r=b) = \frac{NI}{2\pi b} = 1890 \text{ A/m}$$

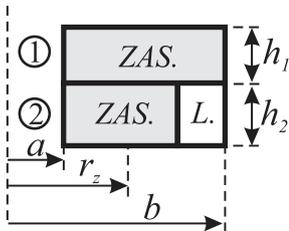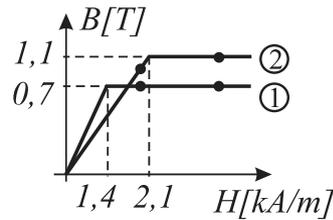Sledi da je materijal 1 u potpunom zasićenju.



$$\Phi = \Phi_1 + \Phi_2$$

$$\Phi_1 = B_{c1} (b-a) h_1 = 0,7 \cdot (0,05 - 0,03) \cdot 0,01$$

$$\boxed{\Phi_1 = 140 \mu\text{Wb}}$$

$$\Phi_2 = B_{c2} (r_z - a) h_2 + \int_a^b \mu_2 \frac{NI}{2\pi r} dr h_2 = B_{c2} (r_z - a) h_2 + \frac{1,1}{2100} \frac{NI}{2\pi} h_2 \ln \frac{b}{r_z}$$

$$\Phi_2 = 1,1 \cdot (0,045 - 0,03) \cdot 0,01 + \frac{1,1}{2100} \frac{170 \cdot 3,49}{2\pi} \cdot 0,01 \cdot \ln \frac{0,05}{0,045}$$


$$\Phi_2 = 165 \mu\text{Wb} + 52,14 \mu\text{Wb}$$

$$\boxed{\Phi_2 = 217,14 \mu\text{Wb}}$$

$$\boxed{\Phi = 357,14 \mu\text{Wb}}$$

K2 Z1

a)

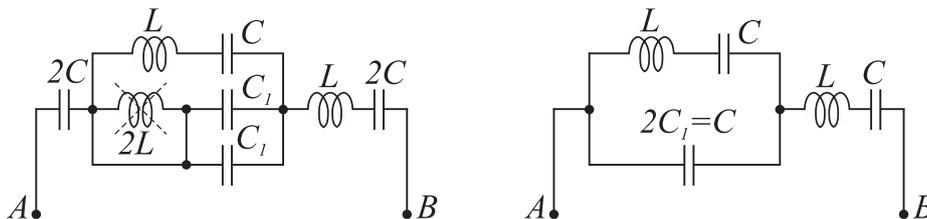

$$\underline{Z}_1 = j\omega L + \frac{1}{j\omega C} = \frac{1 - \omega^2 LC}{j\omega C}$$

$$\underline{Z}_2 = \underline{Z}_1 \parallel \frac{1}{j\omega C} = \frac{\frac{1 - \omega^2 LC}{j\omega C} \cdot \frac{1}{j\omega C}}{\frac{1 - \omega^2 LC}{j\omega C} + \frac{1}{j\omega C}} = \frac{\frac{1 - \omega^2 LC}{j\omega C} \cdot \frac{1}{j\omega C}}{\frac{2 - \omega^2 LC}{j\omega C}} = \frac{1 - \omega^2 LC}{j\omega C(2 - \omega^2 LC)}$$

$$\underline{Z}_{AB} = \underline{Z}_2 + j\omega L + \frac{1}{j\omega C} = \frac{1 - \omega^2 LC}{j\omega C(2 - \omega^2 LC)} + j\omega L + \frac{1}{j\omega C} = \frac{1 - \omega^2 LC}{j\omega C(2 - \omega^2 LC)} + \frac{1 - \omega^2 LC}{j\omega C}$$



$$\underline{Z}_{AB} = \frac{(1 - \omega^2 LC) + (1 - \omega^2 LC)(2 - \omega^2 LC)}{j\omega C(2 - \omega^2 LC)} = \frac{(1 - \omega^2 LC)(3 - \omega^2 LC)}{j\omega C(2 - \omega^2 LC)}$$

$$\underline{Z}_{AB} = -j \frac{(1 - \omega^2 LC)(3 - \omega^2 LC)}{\omega C(2 - \omega^2 LC)}$$

$$\text{Im}\{\underline{Z}_{AB}\} = 0 \Rightarrow \omega_{r1} = \sqrt{\frac{1}{LC}} \quad \omega_{r2} = \sqrt{\frac{3}{LC}}$$

$$\text{Im}\{\underline{Y}_{AB}\} = 0 \Rightarrow \omega_{ar1} = 0 \quad \omega_{ar2} = \sqrt{\frac{2}{LC}} \quad \omega_{ar3} \rightarrow \infty$$

b)

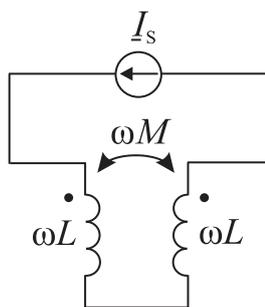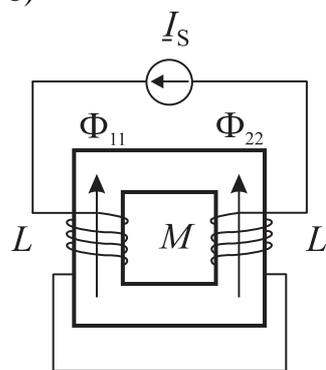

Sprega je negativna.

$$\omega = \omega_{r1} = \sqrt{\frac{1}{LC}} = \sqrt{\frac{1}{20 \cdot 10^{-3} \cdot 5 \cdot 10^{-9}}} = 10^5 \text{ rad/s}$$

$$\underline{Z}_{AB} = 0$$

$$\underline{Z}_L = j\omega L = j10^5 \cdot 20 \cdot 10^{-3} = j2000 \Omega$$

$$\underline{Z}_M = j\omega M = j10^5 \cdot 12 \cdot 10^{-3} = j1200 \Omega$$

b)


$$\underline{U}_s = (\underline{Z}_L \underline{I}_s - \underline{Z}_M \underline{I}_s) + (\underline{Z}_L \underline{I}_s - \underline{Z}_M \underline{I}_s) = (2\underline{Z}_L - 2\underline{Z}_M) \underline{I}_s$$

$$\underline{U}_s = 1,6(1 + j) \text{ V}$$

$$\underline{S} = \underline{U}_s \underline{I}_s^* = j32 \text{ VA}$$

K2 Z2

a)

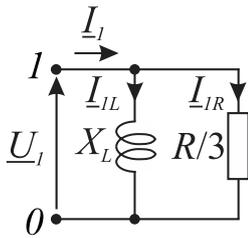

$$I_{1R} = \frac{U_1}{R/3} = \frac{230 e^{j0^\circ}}{10} = 23 e^{j0^\circ} \text{ A} = 23 \text{ A}$$

$$I_{1L} = \frac{U_1}{jX_L} = \frac{230 e^{j0^\circ}}{j20} = \frac{230 e^{j0^\circ}}{20 e^{j90^\circ}} = 11,5 e^{-j90^\circ} \text{ A} = -j11,5 \text{ A}$$

$$I_1 = I_{1R} + I_{1L} = (23 - j11,5) \text{ A} = 25,71 e^{j-26,57^\circ} \text{ A}$$

$$I_2 = I_1 e^{-j120^\circ} = 25,71 e^{-j146,57^\circ} \text{ A}$$

$$I_3 = I_1 e^{-j240^\circ} = 25,71 e^{-j266,57^\circ} \text{ A}$$

$$I_{A1} = |I_{1R}| = 23 \text{ A}$$

$$I_{A2} = |I_{1L}| = 11,5 \text{ A}$$

$$U_{V1} = |U_{12}| = \sqrt{3} |U_1| = \sqrt{3} \cdot 230 = 398,37 \text{ V}$$

$$U_{V2} = |U_3| = 230 \text{ V}$$

$$P_{W1} = \text{Re}\{U_{31} I_3^*\} = U_{31} I_3 \cos \angle(U_{31}, I_3) = \sqrt{3} U_1 I_1 \cos(30^\circ + 26,57^\circ) = \sqrt{3} \cdot 230 \cdot 25,71 \cdot \cos 56,57^\circ$$

$$P_{W1} = 5642,57 \text{ W}$$

$$I_{2L} = I_{1L} e^{-j120^\circ} = 11,5 e^{-j210^\circ} \text{ A}$$

$$P_{W2} = \text{Re}\{U_{31} I_{2L}^*\} = U_{31} I_{2L} \cos \angle(U_{31}, I_{2L}) = \sqrt{3} U_1 I_{1L} \cos 0^\circ = \sqrt{3} \cdot 230 \cdot 11,5 \cdot 1$$

$$P_{W2} = 4581,27 \text{ W}$$

b)

