

Osnovi elektrotehnike 2
(I kolokvijum)

ZADACI


Zadatak 1. Napisati iskaz Bio-Savarovog zakona i primeniti ga pri izračunavanju vektora magnetske indukcije koji u tački A stvaraju:

- krivolinijski deo ravne strujne konture prikazane na slici 1, B_K ;
- pravolinijski delovi iste ravne strujne konture B_P .
- Odrediti poluprečnik r lučnog dela konture, tako da u tački A bude ispunjen uslov $B_K = 4B_P$, pri čemu je $x + r = 2a$.

Sredina je vazduh.

Brojne vrednosti su:

$$I = 5 \text{ A}; a = 5 \text{ cm}, \mu_0 = 4\pi \cdot 10^{-7} \text{ H/m}.$$

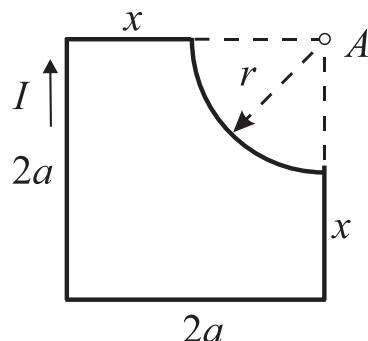


Slika 1.


Zadatak 1. Na slici su prikazani tanko torusno jezgro, permeabilnosti $\mu = 1,4/1000 \text{ H/m}$, sa N gusto i ravnomerno namotanih zavojaka tanke žice (slika 1a), kao i histerezisna petlja materijala od kog je jezgro načinjeno (Slika 1b). Koordinate vrha histerezisne petlje su $H_m=1000 \text{ A/m}$, $B_m=1,4 \text{ T}$. Struja u namotaju je prostoperiodična funkcija vremena $i(t) = I_m \cos(2\pi ft)$. Odrediti:

- u opštim brojevima, izraz za vektor magnetske indukcije,
- izraz za samoinduktivnost namotaja,
- gubitke usled histerezisa nastale u jezgru u intervalu vremena $\Delta t = 5 \text{ minuta}$.

Ostali brojni podaci su: $R = 3 \text{ cm}$, $S = 6 \text{ cm}^2$, $N = 628 \text{ zav}$, $I_m = 0,3 \text{ A}$, $f = 50 \text{ Hz}$.

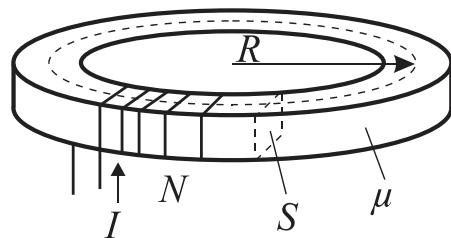

Slika 2a.

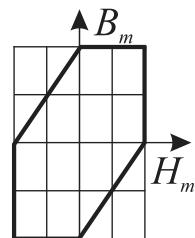

Slika 2b.


PRAVILA POLAGANJA

Za položen kolokvijum neophodno je sakupiti više od 50% od ukupnog broja poena na zadacima. Svaki zadatak se boduje sa 25 poena. Kolokvijum traje jedan sat i trideset minuta.

ZADACI

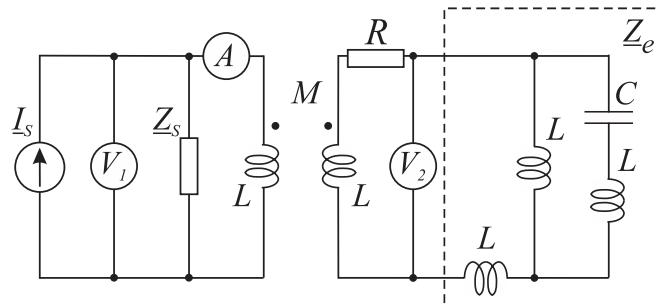Zadatak 1. U mreži prostoperiodične struje prikazanoj na slici 1:

- Odrediti sve rezonantne i antirezonantne kružne učestanosti prijemnika impedanse \underline{Z}_e .
- Ako u kolu strujni generator, I_s , radi na manjoj antirezonantnoj učestanosti, odrediti pokazivanje idealnih mernih instrumenata.
- Odrediti kompleksnu, aktivnu, reaktivnu i prividnu snagu strujnog generatora I_s .




Brojni podaci su: $I_s = (1+j) \text{ A}$, $L = 20 \text{ mH}$, $C = 250 \text{ nF}$, $M = 10 \text{ mH}$, $R = 50 \Omega$, $Z_s = (50-j100) \Omega$.

Slika 1.

Zadatak 2. Na slici 2 je prikazan simetričan trofazni prijemnik impedanse $\underline{Z} = (60+j180) \Omega$, priključen na mrežu faznog napona $U_1 = 230 \text{ V}$.

- Odrediti pokazivanja idealnih mernih instrumenata pre priključivanja kondenzatora.
- Odrediti reaktanse kondenzatora koje je potrebno povezati sa prijemnikom da bi mu se faktor snage popravio na jedinicu.
- Odrediti pokazivanja idealnih mernih instrumenata posle priključivanja kondenzatora.

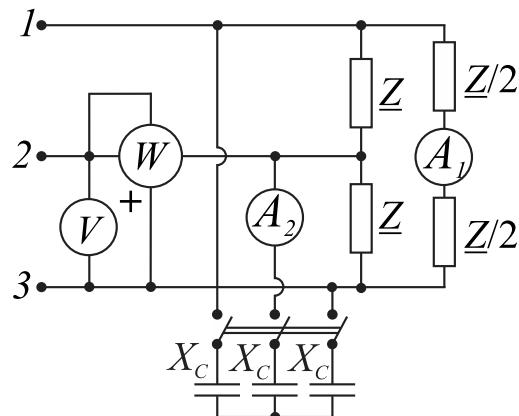


Slika 2.


PRAVILA POLAGANJA

Za položen kolokvijum neophodno je sakupiti više od 50% od ukupnog broja poena na zadacima. Svaki zadatak se bodoje sa 25 poena. Kolokvijum traje jedan sat i trideset minuta.

K1 Z1

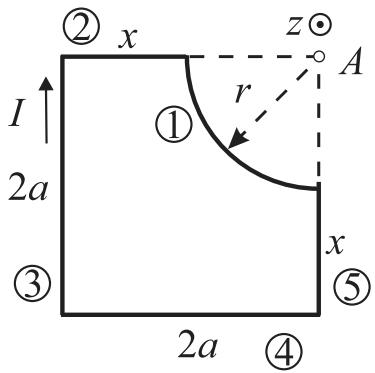

a)

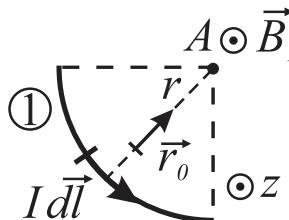

$$d\vec{B} = \frac{\mu_0}{4\pi} \frac{I d\vec{l} \times \vec{r}_0}{r^2}$$

$$dB_1 = \frac{\mu_0}{4\pi} \frac{I dl}{a^2} \quad \alpha(\vec{dl}, \vec{r}_0) = \frac{\pi}{2}$$

$$B_1 = \int dB_1 = \frac{\mu_0 I}{4\pi r^2} \int_0^{1/2r\pi} dl = \frac{\mu_0 I}{4\pi r^2} \frac{1}{2} r\pi = \frac{\mu_0 I}{8r}$$


$$\boxed{\vec{B}_K = \frac{\mu_0 I}{8r} \cdot \vec{i}_z}$$

b)

$$\boxed{\vec{B}_2 = 0}$$

$$\boxed{\vec{B}_5 = 0}$$

$$\sin \alpha(\vec{dl}, \vec{r}_0) = 0$$

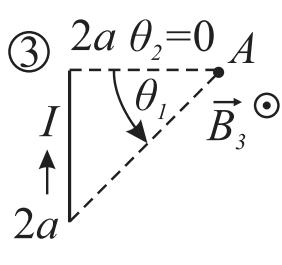


$$d = 2a, \quad \theta_1 \rightarrow -\frac{\pi}{4}, \quad \theta_2 = 0$$

$$B_3 = \frac{\mu_0 I}{4\pi d} (\sin \theta_2 - \sin \theta_1) = \frac{\mu_0 I}{4\pi \cdot 2a} \left[0 - \left(-\frac{\sqrt{2}}{2} \right) \right] = \frac{\mu_0 I \sqrt{2}}{16\pi a}$$

$$\boxed{\vec{B}_3 = \frac{\mu_0 I \sqrt{2}}{16\pi a} \cdot (-\vec{i}_z)}$$
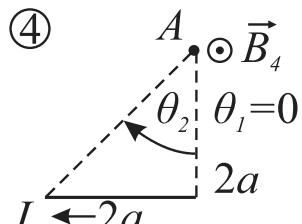
$$d = a, \quad \theta_1 = 0, \quad \theta_2 = \frac{\pi}{4}$$



$$B_4 = \frac{\mu_0 I}{4\pi d} (\sin \theta_2 - \sin \theta_1)$$

$$B_4 = \frac{\mu_0 I_1}{4\pi \cdot 2a} \left[\frac{\sqrt{2}}{2} - 0 \right] = \frac{\mu_0 I \sqrt{2}}{16\pi a}$$

$$\boxed{\vec{B}_4 = \frac{\mu_0 I \sqrt{2}}{16\pi a} \cdot (-\vec{i}_z) = \vec{B}_3}$$

$$\boxed{\vec{B}_P = \frac{\mu_0 I \sqrt{2}}{8\pi a} \cdot (-\vec{i}_z)}$$

c)

$$B_K = 4B_P$$

$$\frac{\mu_0 I}{8r} = 4 \frac{\mu_0 I \sqrt{2}}{8\pi a} \quad \Rightarrow \quad r = \frac{\pi a}{4\sqrt{2}} = 2,78 \text{ cm}$$

K1 Z2

a)

$$\oint_c \vec{H} \cdot d\vec{l} = NI$$

$$H \cdot 2\pi R = NI$$

$$H = \frac{NI}{2\pi R}$$

$$B = \mu H \Rightarrow B = \mu \frac{NI}{2\pi R}$$

b)

$$I = I_m = 0,3 \text{ A}$$

$$\Phi = N \cdot B \cdot S = N \cdot \mu \cdot \frac{NI}{2\pi R} \cdot S = \mu \cdot \frac{N^2 I}{2\pi R} \cdot S$$

$$L = \frac{\Phi}{I} = \frac{\mu \cdot \frac{N^2 I}{2\pi R} \cdot S}{I} = \mu \cdot \frac{N^2 S}{2\pi R}$$

$$L = \frac{1,4}{1000} \cdot \frac{628^2 \cdot 6 \cdot 10^{-4}}{2\pi \cdot 3 \cdot 10^{-2}}$$

$$[L = 1,75 \text{ H}]$$

c)

$$w_h = 12 \cdot \frac{B_m}{2} \cdot \frac{H_m}{2} = \frac{12}{4} \cdot B_m \cdot H_m = 3\mu H_m^2 = 3\mu \left(\frac{NI_m}{2\pi R} \right)^2$$


$$W_h = f \cdot t \cdot w_h \cdot V$$

$$W_h = f \cdot t \cdot 3\mu \left(\frac{NI_m}{2\pi R} \right)^2 \cdot 2\pi R \cdot S$$

$$W_h = f \cdot t \cdot 3\mu \frac{\left(NI_m \right)^2}{2\pi R} \cdot S$$


$$W_h = 50 \cdot 5 \cdot 60 \cdot 3 \cdot \frac{1,4}{1000} \frac{\left(628 \cdot 0,3 \right)^2}{2\pi \cdot 3 \cdot 10^{-2}} \cdot 6 \cdot 10^{-4}$$

$$[W_h = 7117,92 \text{ J}]$$

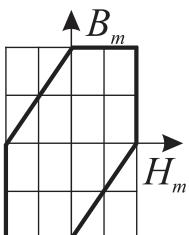

K2 Z1

a)

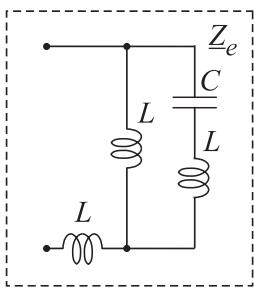

$$\underline{Z}_1 = j\omega L + \frac{1}{j\omega C} = \frac{1 - \omega^2 LC}{j\omega C}$$

$$\underline{Z}_2 = \underline{Z}_1 \parallel j\omega L = \frac{\frac{1 - \omega^2 LC}{j\omega C} j\omega L}{\frac{1 - \omega^2 LC}{j\omega C} + j\omega L} = \frac{j\omega L(1 - \omega^2 LC)}{j\omega C} = \frac{j\omega L(1 - \omega^2 LC)}{1 - 2\omega^2 LC}$$

$$\underline{Z}_e = \underline{Z}_2 + j\omega L = \frac{j\omega L(1 - \omega^2 LC)}{1 - 2\omega^2 LC} + j\omega L = \frac{j\omega L(1 - \omega^2 LC) + j\omega L(1 - 2\omega^2 LC)}{1 - 2\omega^2 LC}$$

$$\underline{Z}_e = j \frac{\omega L(2 - 3\omega^2 LC)}{1 - 2\omega^2 LC}$$

$$\text{Im}\{\underline{Z}_P\} = 0 \Rightarrow \omega L = 0 \quad [\omega_{r1} = 0]$$


$$\text{Im}\{\underline{Y}_P\} = 0 \Rightarrow 1 - 2\omega^2 LC = 0$$

$$\omega_{ar1} = \frac{1}{\sqrt{2LC}}$$

$$2 - 3\omega^2 LC = 0 \quad [\omega_{r2} = \sqrt{\frac{2}{3LC}}]$$

$$\omega_{ar2} \rightarrow \infty$$

b)

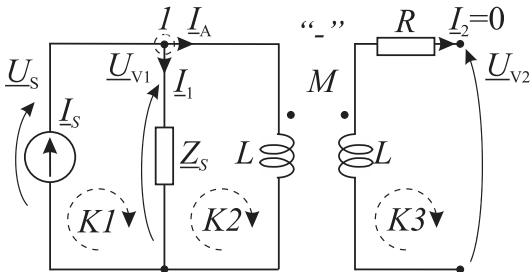

$$\omega_{ar1} = \frac{1}{\sqrt{2LC}} = \frac{1}{\sqrt{2 \cdot 20 \cdot 10^{-3} \cdot 25 \cdot 10^{-9}}} = 10^4 \frac{\text{rad}}{\text{s}} = \omega$$

$$\underline{Z}_e = \infty$$

$$\underline{Z}_L = j\omega L = j10^4 \cdot 20 \cdot 10^{-3} = j200 \Omega$$

$$\underline{Z}_M = j\omega M = j10^4 \cdot 10 \cdot 10^{-3} = j100 \Omega$$

$$\check{C}1: \quad \underline{I}_s = \underline{I}_A + \underline{I}_1$$

$$\underline{I}_A + \underline{I}_1 = 1 + j \quad / \cdot (50 - j100)$$

$$\text{K1:} \quad -\underline{U}_s + \underline{U}_{v1} = 0$$

$$j200\underline{I}_A - (50 - j100)\underline{I}_1 = 0$$

$$\text{K2:} \quad -\underline{Z}_s \underline{I}_1 + \underline{Z}_L \underline{I}_A - \underline{Z}_M \underline{I}_2^0 = 0$$

$$50\underline{I}_A - j100\underline{I}_A + (50 - j100)\underline{I}_1 = 150 - j50$$

$$\text{K3:} \quad \underline{Z}_L \underline{I}_2^0 - \underline{Z}_M \underline{I}_1 + \underline{U}_{v2} = 0$$

$$j200\underline{I}_A - (50 - j100)\underline{I}_1 = 0$$

$$(50 + j100)\underline{I}_A = 150 - j50 \Rightarrow \underline{I}_A = \frac{150 - j50}{50 + j100} = (0, 2 - j1, 4) \text{ A}$$

$$\underline{I}_1 = 1 + j - 0, 2 + j1, 4 = (0, 8 + j2, 4) \text{ A}$$

$$|I_A| = |\underline{I}_A| = 1,41 \text{ A}$$

$$\underline{U}_{v2} = \underline{Z}_M \underline{I}_A = j100 \cdot (0, 2 - j1, 4) = (140 + j20) \text{ V} \quad \Rightarrow \quad |U_{v2}| = |\underline{U}_{v2}| = 141,42 \text{ V}$$

$$\underline{U}_{v1} = \underline{Z}_s \underline{I}_1 = (50 - j100) \cdot (0, 8 + j2, 4) = (280 + j40) \text{ V} \quad \Rightarrow \quad |U_{v1}| = |\underline{U}_{v1}| = 282,84 \text{ V}$$


c)

$$\underline{S}_{IS} = \underline{U}_s \underline{I}_s^* = \underline{U}_{v1} \underline{I}_s^* = (280 + j40) \cdot (1 - j) = (320 - j240) \text{ VA} \quad |\underline{S}_{IS}| = (320 - j240) \text{ VA}$$

$$P_{IS} = 320 \text{ W} \quad Q_{IS} = -240 \text{ VAr} \quad S_{IS} = 400 \text{ VA}$$

K2 Z2

a)

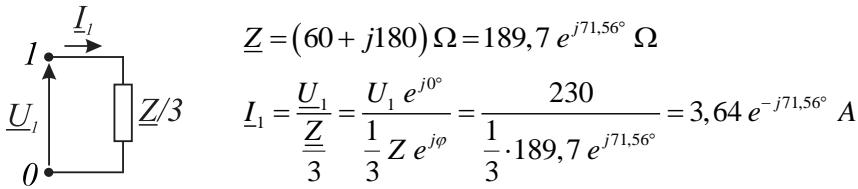

$$U_V^{(a)} = |\underline{U}_{23}| = \sqrt{3} |\underline{U}_1| = \sqrt{3} \cdot 230 = 398,37 V$$


$$I_{A1}^{(a)} = |I_{31}| = \frac{|I_1|}{\sqrt{3}} = \frac{3,64}{\sqrt{3}} = 2,1 A$$

$$I_{A2}^{(a)} = 0$$


$$P_W^{(a)} = \operatorname{Re} \{ \underline{U}_{32} \underline{I}_2^* \} = \underline{U}_{32} \underline{I}_2 \cos \angle(\underline{U}_{32}, \underline{I}_2)$$

$$P_W^{(a)} = \sqrt{3} \underline{U}_1 \underline{I}_1 \underbrace{\cos(120^\circ - 71,56^\circ + 30^\circ)}_{78,44^\circ} = \sqrt{3} \cdot 230 \cdot 3,64 \cdot \cos 78,44^\circ$$

$$P_W^{(a)} = 290,6 W$$

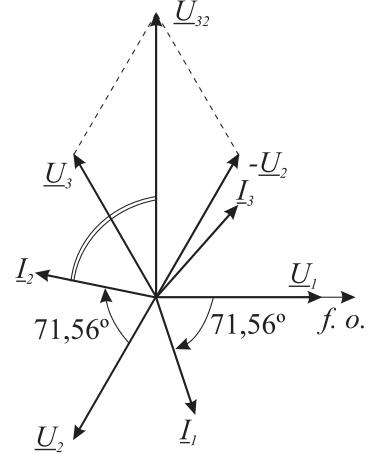

b)

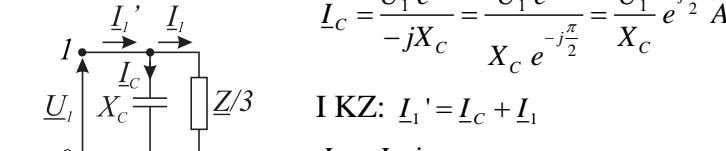

$$\text{IKZ: } \underline{I}_1' = \underline{I}_C + \underline{I}_1$$

$$I_C = I_1 \sin \varphi$$

$$\frac{\underline{U}_1}{X_C} = \frac{\underline{U}_1}{Z/3} \sin \varphi \quad \Rightarrow \quad \frac{1}{X_C} = \frac{3 \sin \varphi}{Z} \quad \Rightarrow \quad X_C = \frac{Z}{3 \sin \varphi} = \frac{189,7}{3 \cdot \sin 71,56^\circ}$$

$$X_C = 66,66 \Omega$$

$$I_1' = I_1 \cos \varphi = 3,64 \cdot \cos 71,56^\circ = 1,15 A$$

$$\underline{I}_1' = 1,15 e^{j0^\circ} A$$

$$I_C = I_1 \sin \varphi = 3,64 \cdot \sin 71,56^\circ = 3,45 A$$

c)

$$U_V^{(c)} = U_V^{(a)} = |\underline{U}_{23}| = 398,37 V$$

$$I_{A1}^{(c)} = I_{A1}^{(a)} = |I_{31}| = 2,1 A$$

$$I_{A2}^{(c)} = |I_{C2}| = 3,45 V$$

$$P_W^{(c)} = \operatorname{Re} \{ \underline{U}_{32} \underline{I}_2'^* \} = \underline{U}_{23} \underline{I}_2' \cos \angle(\underline{U}_{32}, \underline{I}_2')$$

$$P_W^{(c)} = \sqrt{3} \underline{U}_1 \underline{I}_1' \underbrace{\cos(120^\circ + 30^\circ)}_{150^\circ} = \sqrt{3} \cdot 230 \cdot 1,15 \cdot \left(-\frac{\sqrt{3}}{2} \right)$$

$$P_W^{(c)} = -396,75 W$$

