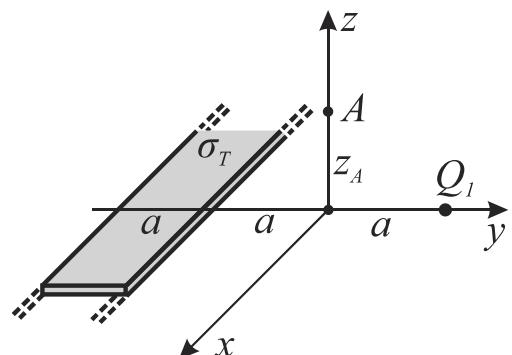


ZADACI

Zadatak 1. Tanka, veoma dugačka, traka od dielektrika, širine a , ravnomerno je nanelektrisana površinskim nanelektrisanjem σ_T . Traka je postavljena u x - y ravni Dekartovog koordinatnog sistema, paralelno sa x osom, kao što je prikazano na slici 1.

- Odrediti izraz za vektor jačine električnog polja koji u tački A , koja se nalazi na z osi, na visini z_A , stvara nanelektrisana traka.
- Odrediti intenzitet sile kojom traka i tačkasto nanelektrisanje, nanelektrisano sa Q_1 , deluju na malo probno nanelektrisanje, Q_P , postavljeno u tačku A . Tačkasto nanelektrisanje Q_1 se nalazi na y osi.

Brojni podaci su: $a = z_A = 1 \text{ cm}$, $\sigma_T = 10 \mu\text{C}/\text{m}^2$, $Q_1 = 20 \text{ nC}$, $Q_P = 1 \text{ pC}$, $\epsilon_0 = 8,85 \cdot 10^{-12} \text{ F/m}$.




Slika 1.

$$\int \tan \alpha \, d\alpha = -\ln |\cos \alpha|$$

Zadatak 2. Koaksijalni kabl poluprečnika elektroda a i b , dužine L , ispunjen je do visine x čvrstim dielektrikom relativne permitivnosti ϵ_{r2} , dok je ostatak kabla ispunjen tečnim dielektrikom relativne permitivnosti ϵ_{r1} . KABL JE PRIKLJUČEN NA IZVOR NAPONA $U = 1 \text{ kV}$ I POSTAVLJEN U VERTIKALNI POLOŽAJ, KAO ŠTO JE PRIKAZANO NA SЛИCI 2.

- Izvesti izraz za kapacitivnost kabla.
- Ako se, kroz odgovarajući otvor na kablu, nivo tečnog dielektrika u njemu smanji za 50%, kapacitivnost kondenzatora se smanji za 10%. Odrediti nivo čvrstog dielektrika, x .
- Izračunati količinu nanelektrisanja na oblogama kondenzatora, nakon smanjenja nivoa tečnog dielektrika za 50%.

Brojni podaci su: $a = 1 \text{ mm}$, $b = 2,7a$, $L = 10 \text{ cm}$, $\epsilon_{r1} = 2$, $\epsilon_{r2} = 3$.

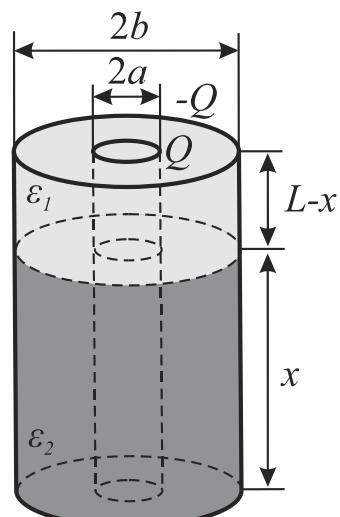

Slika 2.

PRAVILA POLAGANJA

Za položen kolokvijum neophodno je sakupiti više od 50% poena na svakom od zadataka. Svaki zadatak se boduje sa 25 poena. Kolokvijum traje dva sata.


ZADACI

Zadatak 1. U kolu vremenski konstantne struje sa slike 1 izračunati:

- nanelektrisanja kondenzatora Q_1 i Q_2 ,
- jačinu struje I ,
- snagu generatora ems E_6 .

Pri rešavanju kola primeniti metodu sa najmanjim brojem jednačina.

Brojni podaci: $R = 10 \Omega$, $I_s = 0,5 A$, $E_1 = 2 V$, $E_2 = 8 V$, $E_3 = 6 V$, $E_4 = 3 V$, $E_5 = E_6 = 4 V$, $C_1 = C_2 = 5 \mu F$.

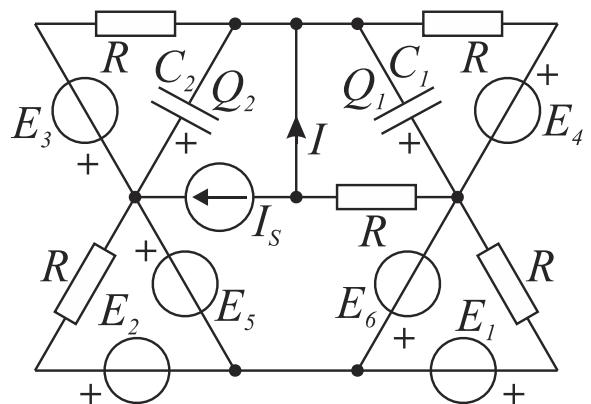


Slika 1.

Zadatak 2. Kada se u simetričnoj mreži sa slike 2, preklopnik prebaci iz položaja (1) u položaj (2), napon između tačaka A i B se poveća za $\Delta U_{AB} = 7 V$.

- Primenjujući teoremu superpozicije, izračunati jačinu struje strujnog generatora, I_{s1} .
- Izračunati snagu strujnog generatora I_{s1} , i snagu naponskog generatora ems E , kada je preklopnik u položaju (2).
- Izračunati pokazivanje idealnog ampermetra, kada je preklopnik u položaju (2).

Brojni podaci su: $R = 35 \Omega$, $E = 6 V$, $I_s = 100 mA$.

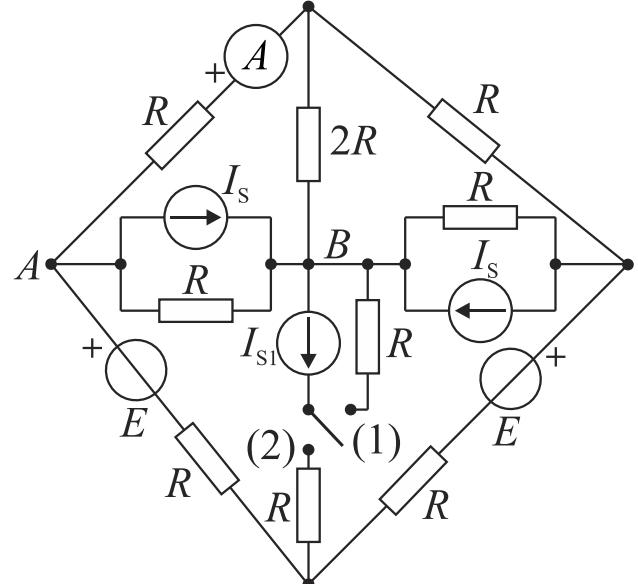


Slika 2.

PRAVILA POLAGANJA

Za položen kolokvijum neophodno je sakupiti više od 50% poena na svakom od zadataka. Svaki zadatak se bodoje sa 25 poena. Kolokvijum traje dva sata.

I-1


a)

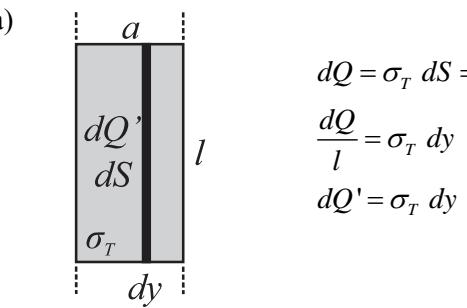

$$dQ = \sigma_T dS = \sigma l dy \quad (l \rightarrow \infty)$$

$$\frac{dQ}{l} = \sigma_T dy$$

$$dQ' = \sigma_T dy$$

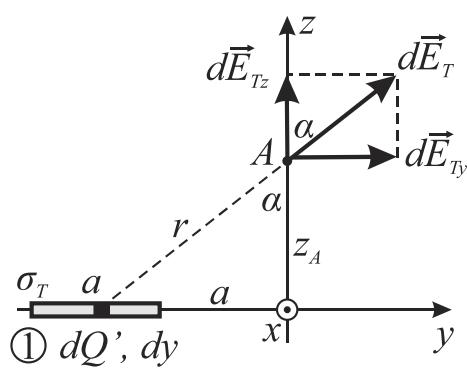

$$dE_T = \frac{dQ'}{2\pi\epsilon_0 r} = \frac{\sigma_T dy}{2\pi\epsilon_0 r}$$

$$dE_{Ty} = dE_T \sin \alpha = \frac{\sigma_T dy}{2\pi\epsilon_0 r} \sin \alpha = \frac{\sigma_T}{2\pi\epsilon_0 r} \frac{r d\alpha}{\cos \alpha} \sin \alpha = \frac{\sigma_T}{2\pi\epsilon_0} \tan \alpha d\alpha$$

$$E_{Ty} = \int dE_{Ty} = \frac{\sigma_T}{2\pi\epsilon_0} \int_{\alpha_{\min}}^{\alpha_{\max}} \tan \alpha d\alpha = \frac{\sigma_T}{2\pi\epsilon_0} (-\ln |\cos \alpha|) \Big|_{\alpha_{\min}}^{\alpha_{\max}}$$

$$E_{Ty} = \frac{\sigma_T}{2\pi\epsilon_0} (\ln |\cos \alpha_{\min}| - \ln |\cos \alpha_{\max}|) = \frac{\sigma_T}{2\pi\epsilon_0} \ln \frac{|\cos \alpha_{\min}|}{|\cos \alpha_{\max}|}$$

$$E_{Ty} = \frac{\sigma_T}{2\pi\epsilon_0} \ln \frac{\frac{z_A}{\sqrt{z_A^2 + a^2}}}{\frac{z_A}{\sqrt{z_A^2 + (2a)^2}}} = \frac{\sigma_T}{2\pi\epsilon_0} \ln \frac{\frac{a}{\sqrt{a^2 + a^2}}}{\frac{a}{\sqrt{a^2 + (2a)^2}}} = \frac{\sigma_T}{2\pi\epsilon_0} \ln \frac{\sqrt{5}}{\sqrt{2}}$$

$$E_{Ty} = \frac{\sigma_T}{2\pi\epsilon_0} \ln \frac{\sqrt{5}}{\sqrt{2}}$$

$$\vec{E}_{Ty} = E_{Ty} \cdot \vec{i}_y$$

$$dE_{Tz} = dE_T \cos \alpha = \frac{\sigma_T dy}{2\pi\epsilon_0 r} \cos \alpha = \frac{\sigma_T}{2\pi\epsilon_0 r} \frac{r d\alpha}{\cos \alpha} \cos \alpha = \frac{\sigma_T}{2\pi\epsilon_0} d\alpha$$


$$E_{Tz} = \int dE_{Tz} = \frac{\sigma_T}{2\pi\epsilon_0} \int_{\alpha_{\min}}^{\alpha_{\max}} d\alpha = \frac{\sigma_T}{2\pi\epsilon_0} \alpha \Big|_{\alpha_{\min}}^{\alpha_{\max}} = \frac{\sigma_T}{2\pi\epsilon_0} (\alpha_{\max} - \alpha_{\min})$$

$$E_{Tz} = \frac{\sigma_T}{2\pi\epsilon_0} \left(\operatorname{arctg} \frac{a+a}{z_A} - \operatorname{arctg} \frac{a}{z_A} \right) E_{Tz} = \frac{\sigma_T}{2\pi\epsilon_0} (\operatorname{arctg} 2 - \operatorname{arctg} 1)$$

$$E_{Tz} = \frac{\sigma_T}{2\pi\epsilon_0} (\operatorname{arctg} 2 - \operatorname{arctg} 1)$$

$$\vec{E}_{Tz} = E_{Tz} \cdot \vec{i}_z$$

b)

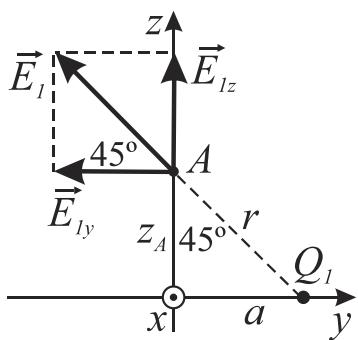

$$E_1 = \frac{Q_l}{4\pi\epsilon_0 r^2} = \frac{Q_l}{4\pi\epsilon_0 (a\sqrt{2})^2} = \frac{Q_l}{8\pi\epsilon_0 a^2}$$

$$E_{1y} = E_1 \cos 45^\circ = \frac{Q_l}{8\pi\epsilon_0 a^2} \cdot \frac{\sqrt{2}}{2}$$

$$E_{1y} = \frac{\sqrt{2} Q_l}{16\pi\epsilon_0 a^2}$$

$$\vec{E}_{1y} = E_{1y} \cdot (-\vec{i}_y)$$

$$E_{1z} = E_1 \sin 45^\circ = \frac{Q_l}{8\pi\epsilon_0 a^2} \cdot \frac{\sqrt{2}}{2}$$

$$E_{1z} = \frac{\sqrt{2} Q_l}{16\pi\epsilon_0 a^2}$$

$$\vec{E}_{1z} = E_{1z} \cdot \vec{i}_z$$


$$\overrightarrow{E}_A = \left(\frac{\sigma_T}{2\pi\varepsilon_0} \ln \frac{\sqrt{5}}{\sqrt{2}} - \frac{\sqrt{2} Q_1}{16\pi\varepsilon_0 a^2} \right) \cdot \vec{i}_y + \left(\frac{\sigma_T}{2\pi\varepsilon_0} (\arctg 2 - \arctg 1) + \frac{\sqrt{2} Q_1}{16\pi\varepsilon_0 a^2} \right) \cdot \vec{i}_z = 0,55 \frac{MV}{m} \cdot \left(-\vec{i}_y \right) + 0,69 \frac{MV}{m} \cdot \vec{i}_z$$

$$F_{na\,Q_P}=Q_P\,E_A=Q_P\,\sqrt{{E_{Ay}}^2+{E_{Az}}^2}=1\cdot 10^{-12}\cdot \sqrt{{\left(0,55\cdot 10^6\right)}^2+{\left(0,69\cdot 10^6\right)}^2}=1\cdot 10^{-12}\cdot 0,88\cdot 10^6=0,88\cdot 10^{-6}\,N$$

$$\boxed{F_{na\,Q_P}=0,88\,\mu N}$$

I-2

a)

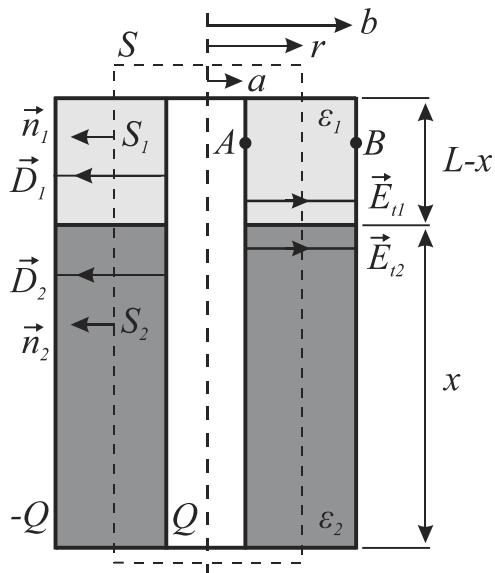

Granični uslov:

$$E_{t1} = E_{t2} \quad E_1 = E_2 = E$$

$$D_{n1} = D_{n2} = 0$$

$$\oint_s \vec{D} \cdot d\vec{s} = Q_{us}$$

$$\int_{S_{OM}} D \, ds = Q$$

$$\int_{OM_1} D_1 \, ds + \int_{OM_2} D_2 \, ds = Q$$

$$D_1 2\pi r(L-x) + D_2 2\pi r x = Q \quad (D_1 = \epsilon_1 E, \quad D_2 = \epsilon_2 E)$$

$$E = \frac{Q}{[\epsilon_1(L-x) + \epsilon_2 x] 2\pi r}, \quad a \leq r \leq b$$

$$U_{AB} = \int_A^B \vec{E} \cdot d\vec{l} = \int_a^b E \, dr = \int_a^b \frac{Q}{[\epsilon_1(L-x) + \epsilon_2 x] 2\pi r} \, dr = \frac{Q}{[\epsilon_1(L-x) + \epsilon_2 x] 2\pi} \ln \frac{b}{a}$$

$$C = \frac{Q}{U_{AB}} = \frac{[\epsilon_1(L-x) + \epsilon_2 x] 2\pi}{\ln \frac{b}{a}} = \frac{(4L+2x)\pi\epsilon_0}{\ln \frac{b}{a}} \quad \epsilon_1 = 2\epsilon_0, \quad \epsilon_2 = 3\epsilon_0$$

b)

$$(L-x)^{NOVO} = \frac{L-x}{2} \Rightarrow C^{NOVO} = 0,9C$$

$$C^{NOVO} = \frac{\left[\epsilon_0 \frac{L-x}{2} + \epsilon_1 \frac{L-x}{2} + \epsilon_2 x \right] 2\pi}{\ln \frac{b}{a}} = \frac{(3L+3x)\pi\epsilon_0}{\ln \frac{b}{a}}$$

$$\frac{(3L+3x)\pi\epsilon_0}{\ln \frac{b}{a}} = 0,9 \cdot \frac{(4L+2x)\pi\epsilon_0}{\ln \frac{b}{a}}$$

$$3L+3x = 0,9 \cdot (4L+2x)$$

$$3L+3x = 3,6L+1,8x$$

$$1,2x = 0,6L$$

$$x = \frac{L}{2} = 5 \text{ cm}$$

c)



$$C^{NOVO} = \frac{(3L+3x)\pi\epsilon_0}{\ln \frac{b}{a}} = \frac{\left(3L+3 \cdot \frac{L}{2}\right)\pi\epsilon_0}{\ln \frac{b}{a}} = \frac{\frac{9L}{2}\pi\epsilon_0}{\ln \frac{b}{a}} = 12,51 \text{ pF}$$

$$Q^{NOVO} = C^{NOVO} U = 12,51 \cdot 10^{-12} \cdot 1 \cdot 10^3 = 12,51 \cdot 10^{-9} \text{ C}$$

$$Q^{NOVO} = 12,51 \text{ nC}$$

II-1

a)

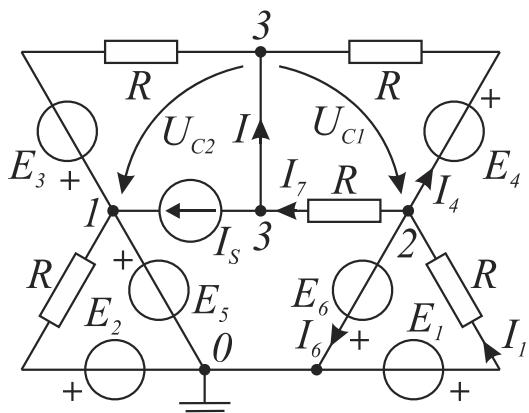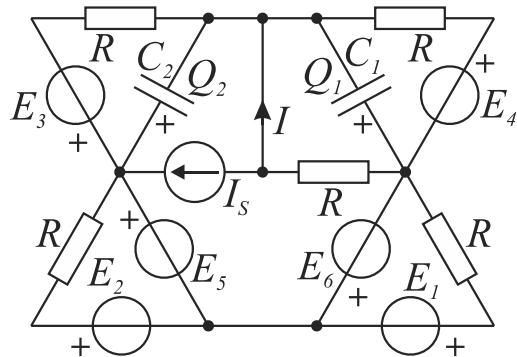

$$\begin{aligned}
 V_1 &= E_5 = 4V \\
 V_2 &= -E_6 = -4V \\
 V_3 & \left(\frac{1}{R} + \frac{1}{R} + \frac{1}{R} \right) - V_1 \left(\frac{1}{R} \right) - V_2 \left(\frac{1}{R} + \frac{1}{R} \right) = -I_s - \frac{E_3}{R} + \frac{E_4}{R} \\
 V_3 \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{10} \right) - 4 \cdot \left(\frac{1}{10} \right) - (-4) \cdot \left(\frac{1}{10} + \frac{1}{10} \right) &= -0,5 - \frac{6}{10} + \frac{3}{10} \quad \cdot 10 \\
 3 \cdot V_3 - 4 \cdot 1 + 4 \cdot 2 &= -5 - 6 + 3 \quad \Rightarrow \quad V_3 = -4V
 \end{aligned}$$

$$Q_1 = C_1 U_{C1} = (V_2 - V_3) C_1 = 0 \mu C$$

$$Q_2 = C_2 U_{C2} = (V_1 - V_3) C_2 = 40 \mu C$$

b)

$$I = I_7 - I_s$$

$$I_7 = \frac{V_2 - V_3}{R} = 0 A$$

$$I = -I_s = -0,5 A$$

c)

$$P_{E_6} = E_6 I_6$$

$$I_6 = I_1 - I_7 - I_4$$

$$I_1 = \frac{-V_2 + E_1}{R} = 0,6 A$$

$$I_4 = \frac{V_2 - V_3 + E_4}{R} = 0,3 A$$

$$I_6 = 0,3 A$$


$$P_{E_6} = 4 \cdot 0,3 = 1,2 W$$

II-2

a)

$$U_{AB}^{(2)} = U_{AB}^{(1)} + U_{AB}', \quad \Rightarrow \quad \Delta U_{AB} = U_{AB}^{(2)} - U_{AB}^{(1)} = U_{AB}' = 7\text{V}$$

Kolo je simetrično.

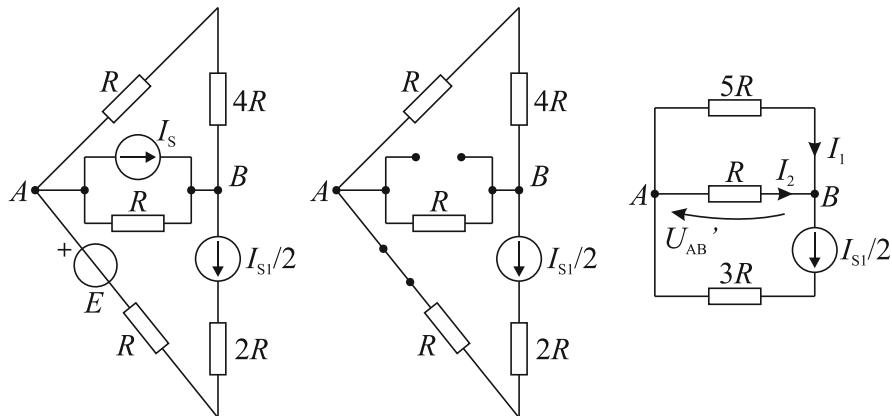


$$I_1 = \frac{U_{AB}'}{5R} = \frac{7}{5 \cdot 35} = 40 \text{ mA}$$

$$I_2 = \frac{U_{AB}'}{R} = \frac{7}{35} = 200 \text{ mA}$$

$$\frac{I_{S1}}{2} = I_1 + I_2 = 240 \text{ mA}$$

$$I_{S1} = 480mA$$

b)

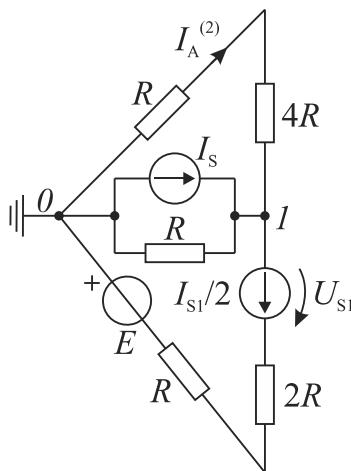

$$\begin{aligned} V_0 &= 0 \text{ V} \\ \hline V_1 & \left(\frac{1}{5R} + \frac{1}{\infty} + \frac{1}{R} + \frac{1}{3R+\infty} \right) = I_S - \frac{I_{S1}}{2} \\ \hline V_1 & \left(\frac{1}{5 \cdot 35} + \frac{1}{35} \right) = 100m - 240m & / \cdot 5 \cdot 35 \\ \hline 6V_1 & = -24,5 \quad \Rightarrow \quad V_1 = -4,08 \text{ V} \end{aligned}$$

$$U_{s1} = 2R \frac{I_{s1}}{2} + R \frac{I_{s1}}{2} - E + U_{01} = 23,283V$$

$$P_{S1} = U_{S1} I_{S1} = 23,283 \cdot 480 m$$

$$P_{S1} = 11,176 \text{ W}$$

$$P_E = EI_E = E \frac{I_{S1}}{2}$$

$$P_E = 1,44 \text{ W}$$

c)

$$I_A^{(2)} = \frac{V_0 - V_1}{R + 4R} = \frac{4,08}{5 \cdot 35}$$

$$I_A^{(2)} = 23,31 \text{ mA}$$