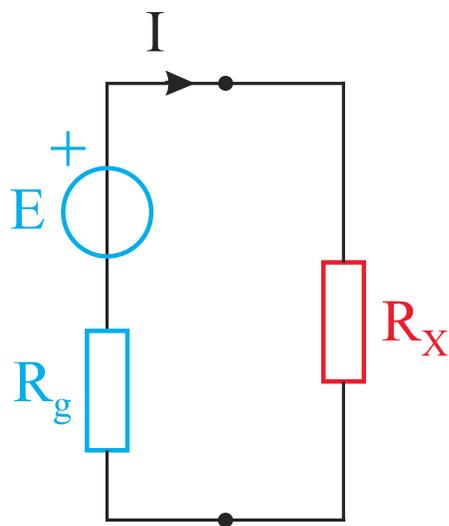


Petak, 10.12.2021.

Vežbe 18

Vremenski konstantne
električne struje

Uslov prenosa maksimalne snage:
(snaga pretvaranja električne energije u toplotu)



$$I = \frac{E}{R_g + R_X}$$

$$P_{RX} = R_X \cdot I^2 = R_X \cdot \left(\frac{E}{R_g + R_X} \right)^2 = \frac{R_X}{(R_g + R_X)^2} \cdot E^2$$

$$\frac{\partial P_{RX}}{\partial R_X} = \frac{1 \cdot (R_g + R_X)^2 - R_X \cdot 2 \cdot (R_g + R_X) \cdot 1}{(R_g + R_X)^4} \cdot E^2$$


$$\frac{\partial P_{RX}}{\partial R_X} = 0 \quad \Rightarrow \quad P_{RX}^{max}$$

$$\frac{\partial P_{RX}}{\partial R_X} = 0 \quad (R_g + R_X)^2 - 2 \cdot R_X \cdot (R_g + R_X) = 0$$

$$(R_g + R_X) \cdot (R_g + R_X - 2 \cdot R_X) = 0$$

$$R_g - R_X = 0$$

$$\boxed{R_X = R_g}$$

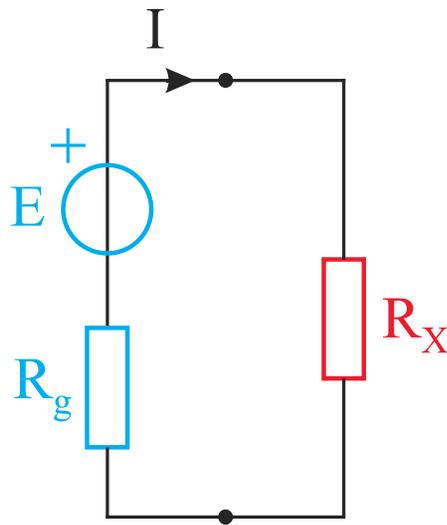

Za $R_X = R_g :$

$$P_{RX} = P_{RX}^{max} = \frac{R_g}{(R_g + R_g)^2} \cdot E^2$$

$$P_{RX}^{max} = \frac{E^2}{4 \cdot R_g}$$


$$P_{Rg} = R_g \cdot I^2 = R_g \cdot \left(\frac{E}{R_g + R_X} \right)^2 = \frac{R_g}{(R_g + R_X)^2} \cdot E^2$$

$$P_E = E \cdot I = E \cdot \frac{E}{R_g + R_X} = \frac{1}{R_g + R_X} \cdot E^2$$

Zadatak 1. Prijemnik promenljive otpornosti R_p je priključen na generator elektromotorne sile $E=6\text{ V}$ i unutrašnje otpornosti $R_g=2\ \Omega$. Otpornost prijemnika se menja u granicama od $0\ \Omega \leq R_p \leq 10\ \Omega$.

- a) Na istom dijagramu prikazati grafički, kako se u funkciji otpornosti R_p menjaju: snaga prijemnika P_{RP} , snaga generatora P_E i snaga Džulovih gubitaka u generatoru P_{Rg} .
- b) Skicirati grafik promene jačine struje u kolu u funkciji otpornosti R_p .

a)

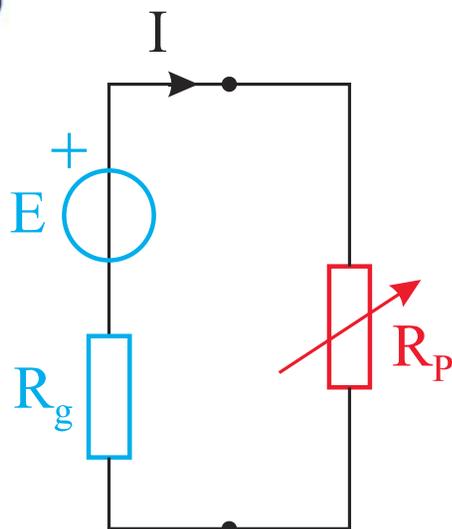


$$I = \frac{E}{R_g + R_p}$$

$$P_{RP} = R_p \cdot I^2 = R_p \cdot \left(\frac{E}{R_g + R_p} \right)^2 = \frac{R_p}{(R_g + R_p)^2} \cdot E^2$$

$$P_{Rg} = R_g \cdot I^2 = R_g \cdot \left(\frac{E}{R_g + R_p} \right)^2 = \frac{R_g}{(R_g + R_p)^2} \cdot E^2$$

$$P_E = E \cdot I = E \cdot \frac{E}{R_g + R_p} = \frac{1}{R_g + R_p} \cdot E^2$$

R_P [Ω]	0	1	2	3	4	6	8	10
P_{RP} [W]	0	4	4,5	4,32	4	3,375	2,88	2,5
P_{Rg} [W]	18	8	4,5	2,88	2	1,125	0,72	0,5
P_E [W]	18	12	9	7,2	6	4,5	3,6	3
I [A]	3	2	1,5	1,2	1	0,75	0,6	0,5

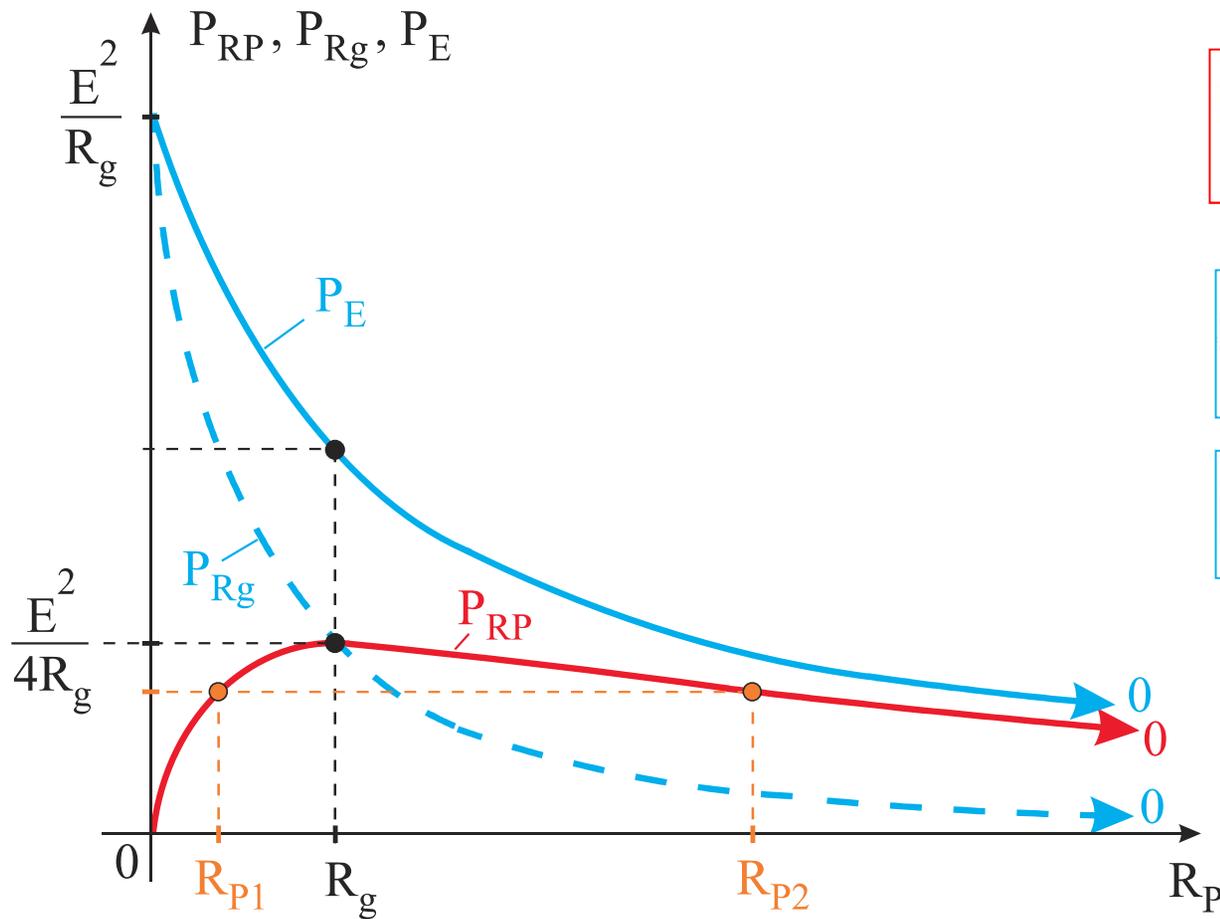


$$P_{RP} = \frac{R_P}{(R_g + R_P)^2} \cdot E^2$$

$$P_{Rg} = \frac{R_g}{(R_g + R_P)^2} \cdot E^2$$

$$P_E = \frac{1}{R_g + R_P} \cdot E^2$$

b)

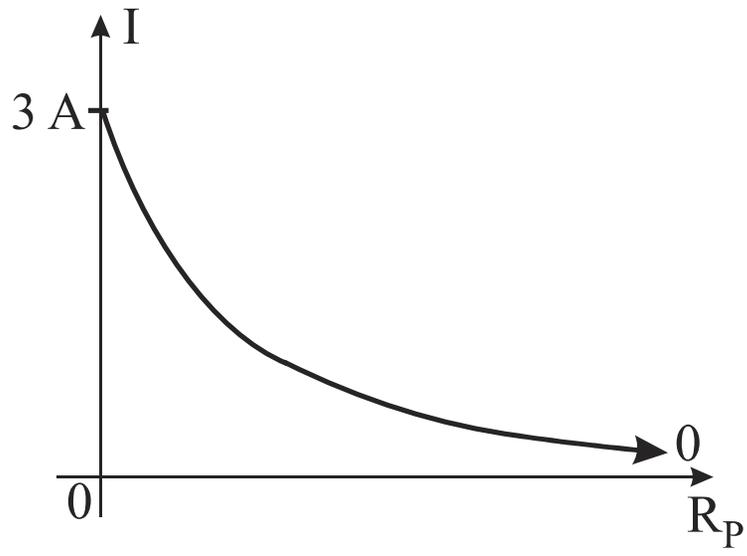

Zadatak 2. Stepen iskorišćenja.

$$P_{RP} = \frac{R_p}{(R_g + R_p)^2} \cdot E^2$$

$$P_{Rg} = \frac{R_g}{(R_g + R_p)^2} \cdot E^2$$

$$P_E = \frac{1}{R_g + R_p} \cdot E^2$$

$$\eta = \frac{P_{korisno}}{P_{utrošeno}} = \frac{P_{RP}}{P_E} = \frac{\frac{R_p}{(R_g + R_p)^2} \cdot E^2}{\frac{1}{R_g + R_p} \cdot E^2} = \frac{R_p}{R_g + R_p}$$


$$R_g = 2 \Omega$$

$$1.) \quad R_p = 1 \Omega \quad \eta = \frac{1}{2+1} = 0,33 \quad \eta(\%) = 33 \%$$


$$2.) \quad R_p = 2 \Omega \quad \eta = \frac{2}{2+2} = 0,5 \quad \eta(\%) = 50 \%$$

$$3.) \quad R_p = 4 \Omega \quad \eta = \frac{4}{2+4} = 0,66 \quad \eta(\%) = 66 \%$$

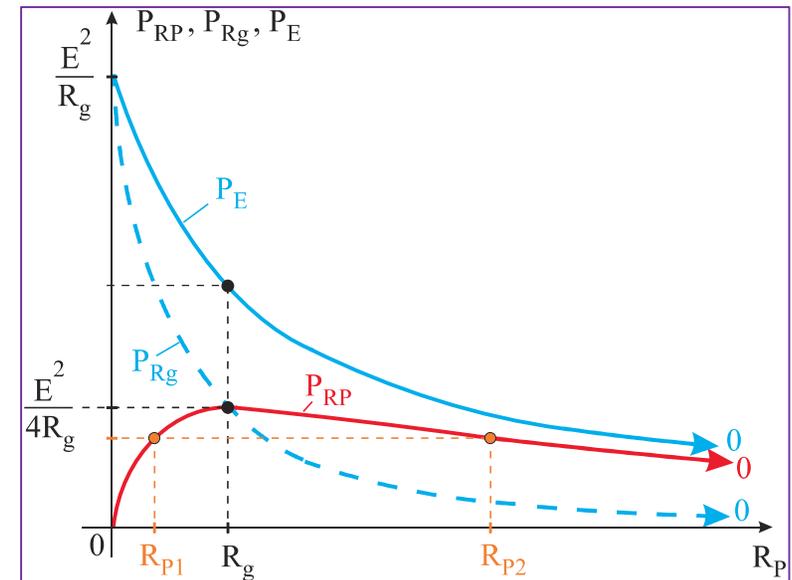$R_p = 4 \Omega$ daje efikasnije prenos energije nego $R_p = 1 \Omega$.



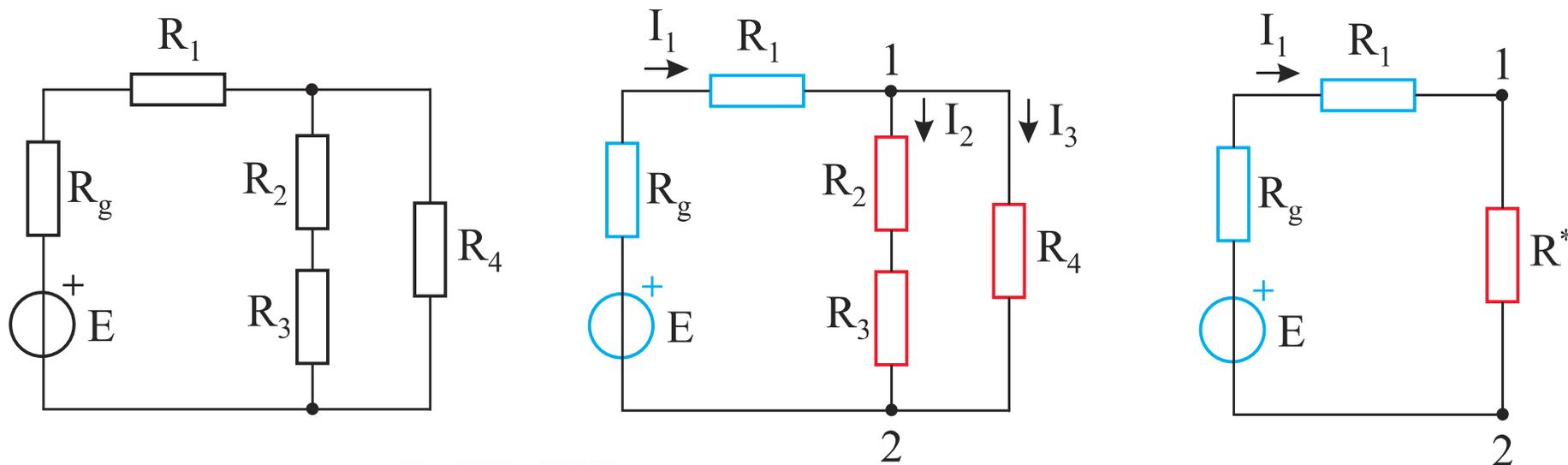Zadatak 3. Odrediti R_4 u mreži prikazanoj na slici, tako da ukupna snaga Džulovih gubitaka u otpornicima R_2 , R_3 i R_4 bude najveća moguća. Odrediti sve vrednosti otpornosti i snagu cele grupe. $E=110\text{ V}$, $R_g=0,5\ \Omega$, $R_1=25\ \Omega$, $R_2=10\ \Omega$, $R_3=35\ \Omega$.





$$R^* = R_4 \parallel (R_2 + R_3) = \frac{R_4 \cdot (R_2 + R_3)}{R_4 + (R_2 + R_3)} = ?$$

Prilagođenje po snazi: $R_g + R_1 = R^* \Rightarrow R^* = 25,5\ \Omega$

$$\frac{R_4 \cdot (10 + 35)}{R_4 + (10 + 35)} = 25,5 \Rightarrow R_4 = 58,85\ \Omega$$

$$P_{R^*} = R^* \cdot I_1^2 = R^* \cdot \left(\frac{E}{(R_1 + R_g) + R^*} \right)^2 = R^* \cdot \frac{E^2}{(2R^*)^2} = \frac{E^2}{4R^*} = \frac{110^2}{4 \cdot 25,5} \Rightarrow P_{R^*} = 118,6\text{ W}$$

Naponski razdelnik:

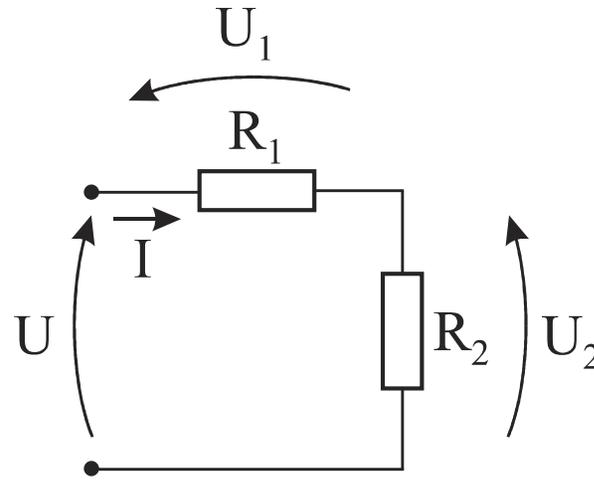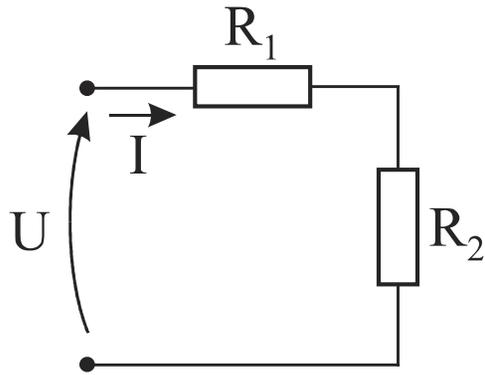

$$I = \frac{U}{R_1 + R_2}$$



$$U_1 = R_1 \cdot I = R_1 \cdot \frac{U}{R_1 + R_2}$$

$$U_1 = \frac{R_1}{R_1 + R_2} \cdot U$$

$$U_2 = R_2 \cdot I = R_2 \cdot \frac{U}{R_1 + R_2}$$

$$U_2 = \frac{R_2}{R_1 + R_2} \cdot U$$

Strujni razdelnik:

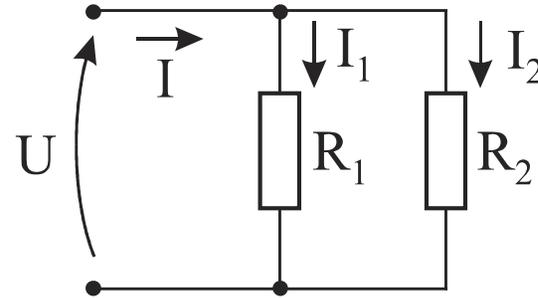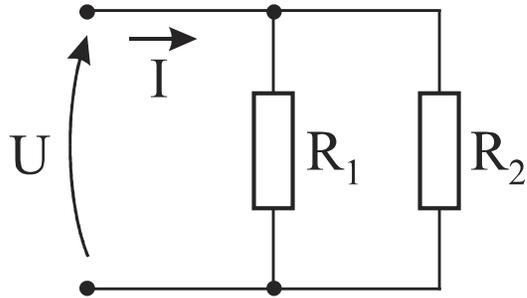

$$U = (R_1 \parallel R_2) \cdot I$$

$$I_1 = \frac{U}{R_1} = \frac{(R_1 \parallel R_2)}{R_1} \cdot I = \frac{R_1 \cdot R_2}{R_1 + R_2} \cdot I$$

$$I_1 = \frac{R_2}{R_1 + R_2} \cdot I$$

$$I_2 = \frac{U}{R_2} = \frac{(R_1 \parallel R_2)}{R_2} \cdot I = \frac{R_1 \cdot R_2}{R_1 + R_2} \cdot I$$

$$I_2 = \frac{R_1}{R_1 + R_2} \cdot I$$