

Osnovi elektrotehnike 2
(I kolokvijum)


K1

18.07.2026.

ZADACI

Zadatak 1. Na slici 1 je prikazan žičani provodnik, sa vremenski konstantnom strujom jačine I . Provodnik se sastoji od četiri pravolinijska i dva lučna segmenta. Tri pravolinijska segmenta leže u x - z ravni Dekartovog pravouglog koordinatnog sistema, dok preostali četvrti leži u x - y ravni, kao što je prikazano na slici. Lučni segmenti leže u x - y ravni: prvi nad uglom α , poluprečnika $2a$, a drugi nad uglom $(\pi - \alpha)$, poluprečnika a . Sredina je vazduh. Odrediti, u opštim brojevima, izraz za vektor magnet-ske indukcije koji u tački O (centar koordinatnog sistema) stvara žičani provodnik.

Brojne vrednosti: $\alpha = \pi/4$, $\mu_0 = 4\pi \cdot 10^{-7} \text{ H/m}$.

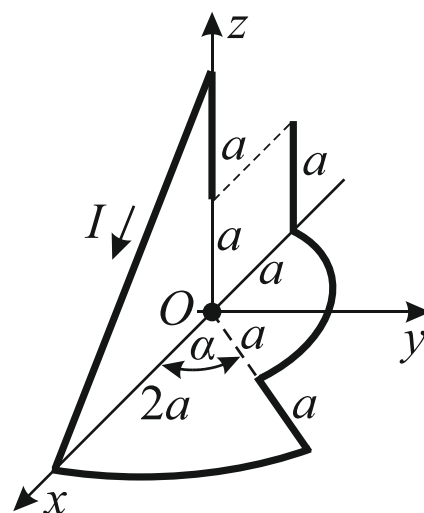


Slika 1.


Zadatak 2. Na slici 2a je prikazano tanko magnetsko kolo, načinjeno od dva feromagnetska materijala čije su idealizovane magnetske karakteristike date na slici 2b. Na jezgro je ravnomerno i gusto namotan pobudni namotaj sa $N = 100$ zavoja u kojima je uspostavljena struja jačine I . Odrediti:

- Intenzitet struje u pobudnom namotaju, I , pri kojoj je vektor magnetske indukcije u vazдушnom procepu jednak $B_0 = 1,2 \text{ T}$. Rasipanja zanemariti.
- Količinu naelektrisanja, q , koja protekne kroz probni zavojak u naznačenom smeru, prilikom uspostavljanja magnet-skog polja u kolu. Zavojak ima jedan namotaj otpornosti $R_Z = 15 \Omega$.
- Magnetsku energiju sadržanu u delu kola načinjenog od materijala 1, pri struji određenoj pod a).

Brojni podaci: $l_1 = 20 \text{ cm}$, $l_2 = 10 \text{ cm}$, $l_0 = 1 \text{ mm}$, $S_1 = 1 \text{ cm}^2$, $S_2 = 2 \text{ cm}^2$.

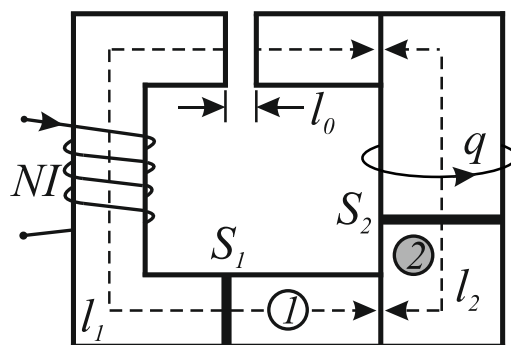

Slika 2a.

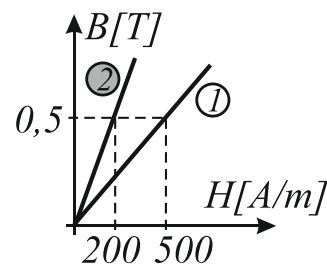

Slika 2b.

PRAVILA POLAGANJA

Za položen kolokvijum neophodno je sakupiti više od 50% poena na svakom od zadataka. Svaki zadatak se boduje sa 25 poena. Kolokvijum traje jedan sat i trideset minuta.

Osnovi elektrotehnike 2
(II kolokvijum)

K2


18.07.2026.

ZADACI

Zadatak 1. U mreži prostoperiodične struje prikazanoj na slici 1:

- Odrediti sve rezonantne kružne učestanosti prijemnika impedanse $\underline{Z}_P$.
- Odrediti pokazivanja idealnih mernih instrumenata, u situaciji kada je ugaona učestanost generatora elektromotorne sile $\underline{E}$ jednaka manjoj rezonantnoj učestanosti prijemnika $\underline{Z}_P$.
- Odrediti reaktivnu snagu generatora $\underline{E}$, pri ugaonoj učestanosti pod b).

Brojni podaci: $C = 100 \mu F$, $L = 30 mH$,
 $C_1 = 4C$, $L_1 = 2L$, $R = 15 \Omega$, $\underline{E} = (15 + j5) V$.

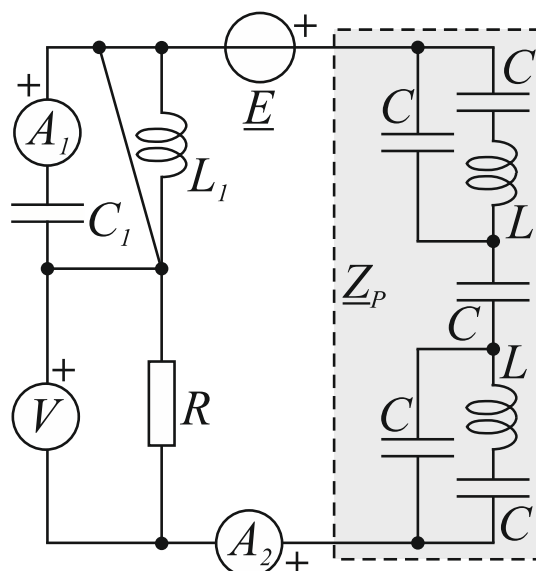


Slika 1.

Zadatak 2. Trofazni prijemnik, sastavljen od otpornika otpornosti R i kondenzatora reaktanse X_C , priključen je na sekundar trofaznog transformatora, kao što je prikazano na slici 2. Primar transformatora je priključen na trofaznu, simetričnu mrežu faznog napona prve faze $\underline{U}_A = 230 V$.

- Izračunati kompleksne jačine struja primara i sekundara.
- Odrediti pokazivanja idealnih mernih instrumenata.
- Na istom fazorskom dijagramu prikazati fazore faznih napona primara i fazore svih veličina od kojih zavise pokazivanja idealnih mernih instrumenata.

Brojne vrednosti: $R = 15 \Omega$, $X_C = 60 \Omega$,
 $X_L = 20 \Omega$, $X_M = 10 \Omega$.

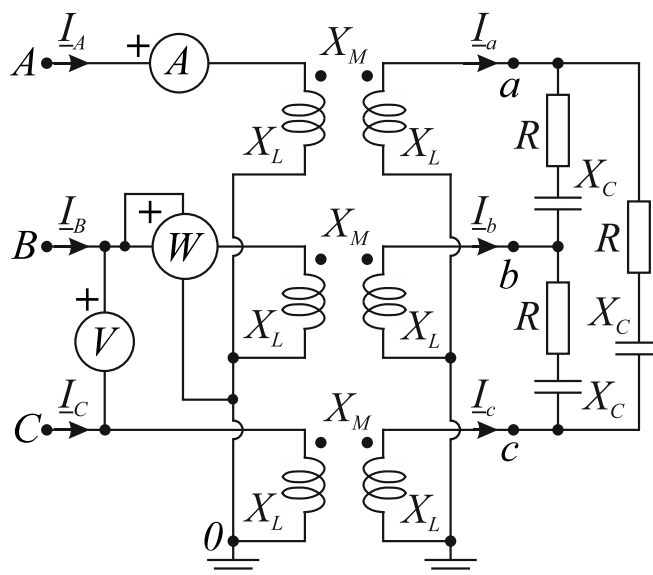


Slika 2.

PRAVILA POLAGANJA

Za položen kolokvijum neophodno je sakupiti više od 50% poena na svakom od zadataka. Svaki zadatak se boduje sa 25 poena. Kolokvijum traje jedan sat i trideset minuta.

I-1

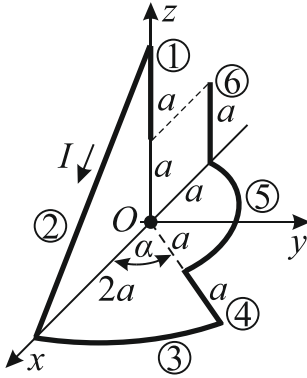


$$\vec{B}_1 = 0$$

$$\sin \angle(\vec{dl}, \vec{r}_0) = 0$$

$$\vec{B}_4 = 0$$


$$\sin \angle(\vec{dl}, \vec{r}_0) = 0$$

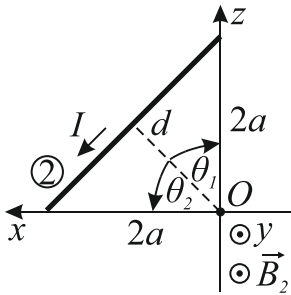

$$[2] \quad d = a\sqrt{2}, \quad \theta_1 = -\frac{\pi}{4}, \quad \theta_2 = \frac{\pi}{4}$$

$$B_2 = \frac{\mu_0 I}{4\pi d} (\sin \theta_2 - \sin \theta_1) = \frac{\mu_0 I}{4\pi a\sqrt{2}} \left[\frac{\sqrt{2}}{2} - \left(-\frac{\sqrt{2}}{2} \right) \right] = \frac{\mu_0 I}{4\pi a}$$

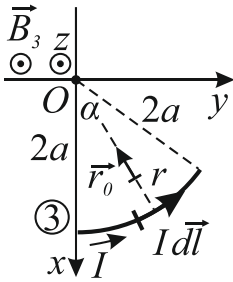
$$\vec{B}_2 = \frac{\mu_0 I}{4\pi a} \cdot \vec{i}_y$$



$$d\vec{B}_3 = \frac{\mu_0}{4\pi} \frac{I \vec{dl} \times \vec{r}_0}{r^2} \quad dB_3 = \frac{\mu_0}{4\pi} \frac{I dl}{(2a)^2} \quad \angle(\vec{dl}, \vec{r}_0) = \frac{\pi}{2} \quad \left(\alpha = \frac{\pi}{4} \right)$$

$$B_3 = \int dB_3 = \frac{\mu_0 I}{16\pi a^2} \int_0^{\frac{1}{8} 2\pi} dl = \frac{\mu_0 I}{16\pi a^2} \frac{a\pi}{2} = \frac{\mu_0 I}{32a}$$

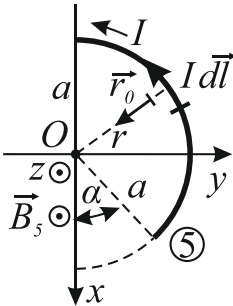
$$\vec{B}_3 = \frac{\mu_0 I}{32a} \cdot \vec{i}_z$$



$$d\vec{B}_5 = \frac{\mu_0}{4\pi} \frac{I \vec{dl} \times \vec{r}_0}{r^2} \quad dB_5 = \frac{\mu_0}{4\pi} \frac{I dl}{a^2} \quad \angle(\vec{dl}, \vec{r}_0) = \frac{\pi}{2} \quad \left(\alpha = \frac{\pi}{4} \right)$$

$$B_5 = \int dB_5 = \frac{\mu_0 I}{4\pi a^2} \int_0^{\frac{3}{8} 2\pi} dl = \frac{\mu_0 I}{4\pi a^2} \frac{3a\pi}{4} = \frac{3\mu_0 I}{16a}$$
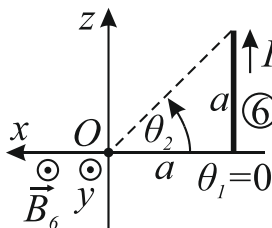
$$\vec{B}_5 = \frac{3\mu_0 I}{16a} \cdot \vec{i}_z$$




$$[6] \quad d = a, \quad \theta_1 = 0, \quad \theta_2 = \frac{\pi}{4}$$

$$B_6 = \frac{\mu_0 I}{4\pi d} (\sin \theta_2 - \sin \theta_1) = \frac{\mu_0 I}{4\pi a} \left(\frac{\sqrt{2}}{2} - 0 \right) = \frac{\sqrt{2}\mu_0 I}{8\pi a}$$

$$\vec{B}_6 = \frac{\sqrt{2}\mu_0 I}{8\pi a} \cdot \vec{i}_y$$

$$\vec{B}_O = \vec{B}_1 + \vec{B}_2 + \vec{B}_3 + \vec{B}_4 + \vec{B}_5 + \vec{B}_6 = \left(\frac{\mu_0 I}{4\pi a} + \frac{\sqrt{2}\mu_0 I}{8\pi a} \right) \cdot \vec{i}_y + \left(\frac{\mu_0 I}{32a} + \frac{3\mu_0 I}{16a} \right) \cdot \vec{i}_z$$

I-2

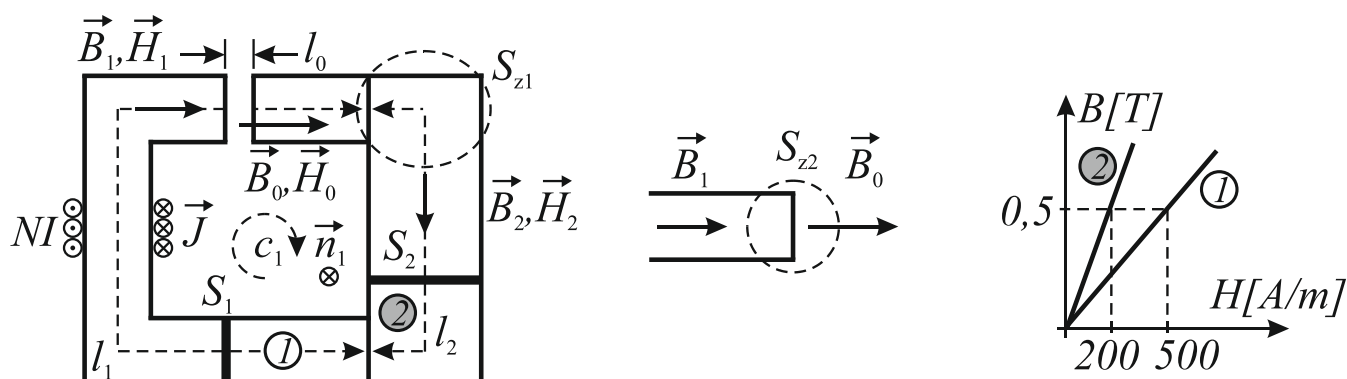

a)

$$\oint_c \vec{H} \cdot d\vec{l} = NI$$

$$c_1: H_1 l_1 + H_0 l_0 + H_2 l_2 = NI \quad (1)$$

$$\oint_{S_z} \vec{B} \cdot d\vec{s} = 0$$

$$S_{z1}: -B_1 S_1 + B_2 S_2 = 0 \quad (2)$$

$$S_{z2}: -B_1 S_1 + B_0 S_0 = 0$$

$$(S_1 = S_0) \quad B_1 = B_0 \quad (3)$$

$$B_0 = 1,2 \text{ T} \Rightarrow H_0 = \frac{B_0}{\mu_0} = \frac{1,2}{4\pi \cdot 10^{-7}} = 955,41 \text{ kA/m}$$


$$\text{Iz (3) sledi: } B_1 = B_0 = 1,2 \text{ T} \Rightarrow H_1 = \frac{B_1}{\mu_1} = \frac{1,2}{\frac{0,5}{500}} = 1200 \text{ A/m}$$

$$\text{Iz (2) sledi: } B_2 = B_1 \frac{S_1}{S_2} = 1,2 \cdot \frac{1 \cdot 10^{-4}}{2 \cdot 10^{-4}} = 0,6 \text{ T} \Rightarrow H_2 = \frac{B_2}{\mu_2} = \frac{0,6}{\frac{0,5}{200}} = 240 \text{ A/m}$$

$$\text{Iz (1) sledi: } I = \frac{H_1 l_1 + H_0 l_0 + H_2 l_2}{N} = \frac{1200 \cdot 0,2 + 955,41 \cdot 10^3 \cdot 1 \cdot 10^{-3} + 240 \cdot 0,1}{100}$$

$$I = 12,2 \text{ A}$$

b)

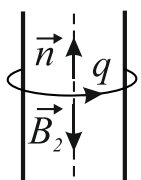

$$q = -\frac{1}{R_z} \left(\Phi_2^{KR} - \Phi_2^{POC^0} \right) = -\frac{1}{R_z} \left(\int_{S_2} \vec{B}_2 \cdot d\vec{s} \right) = -\frac{1}{R_z} (-B_2 S_2)$$

$$\angle(\vec{B}_2, \vec{n}) = \pi$$

$$q = \frac{1}{R_z} B_2 S_2 = \frac{1}{15} \cdot 0,6 \cdot 2 \cdot 10^{-4}$$

$$q = 8 \mu\text{C}$$


c)

$$W_{m1} = w_{m1} V_1 = \frac{1}{2} B_1 H_1 l_1 S_1 = \frac{1}{2} \cdot 1,2 \cdot 1200 \cdot 0,2 \cdot 1 \cdot 10^{-4}$$

$$W_{m1} = 14,4 \text{ mJ}$$

II-1

a)

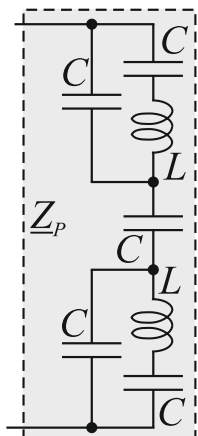

$$Z_1 = j\omega L + \frac{1}{j\omega C} = \frac{1 - \omega^2 LC}{j\omega C}$$

$$Z_2 = Z_1 \parallel \frac{1}{j\omega C} = \frac{\frac{1 - \omega^2 LC}{j\omega C} \cdot \frac{1}{j\omega C}}{\frac{1 - \omega^2 LC}{j\omega C} + \frac{1}{j\omega C}} = \frac{\frac{1 - \omega^2 LC}{j\omega C} \cdot \frac{1}{j\omega C}}{\frac{2 - \omega^2 LC}{j\omega C}} = \frac{1 - \omega^2 LC}{j\omega C(2 - \omega^2 LC)}$$

$$Z_P = Z_2 + \frac{1}{j\omega C} + Z_2 = \frac{1 - \omega^2 LC}{j\omega C(2 - \omega^2 LC)} + \frac{1}{j\omega C} + \frac{1 - \omega^2 LC}{j\omega C(2 - \omega^2 LC)}$$



$$Z_P = \frac{1 - \omega^2 LC}{j\omega C(2 - \omega^2 LC)} + \frac{2 - \omega^2 LC}{j\omega C(2 - \omega^2 LC)} + \frac{1 - \omega^2 LC}{j\omega C(2 - \omega^2 LC)}$$

$$Z_P = -j \frac{4 - 3\omega^2 LC}{\omega C(2 - \omega^2 LC)}$$

$$\text{Im}\{Z_P\} = 0 \Rightarrow \omega_{r1} = \sqrt{\frac{4}{3LC}} \quad \omega_{r2} \rightarrow \infty$$

$$\text{Im}\{Y_P\} = 0 \Rightarrow \omega_{ar1} = 0 \quad \omega_{ar2} = \sqrt{\frac{2}{LC}}$$

b)

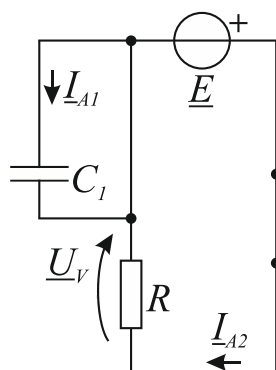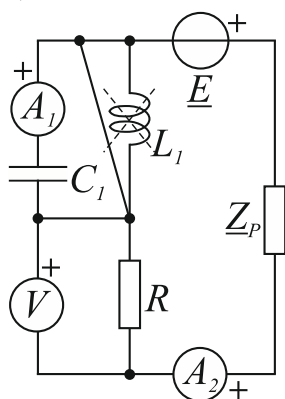

$$\omega = \omega_{r1} = \sqrt{\frac{4}{3LC}} = \sqrt{\frac{4}{3 \cdot 30 \cdot 10^{-3} \cdot 100 \cdot 10^{-6}}} = \frac{2000}{3} \frac{\text{rad}}{\text{s}}$$

$$Z_P = 0$$

$$I_{A1} = \frac{U_{C1}^0}{Z_{C1}} = 0 \text{ A}$$

$$I_{A1} = 0 \text{ A}$$

$$I_{A2} = \frac{E}{R} = \frac{15 + j5}{15} = \left(1 + j\frac{1}{3}\right) \text{ A}$$

$$I_{A2} = |I_{A2}| = \sqrt{1^2 + \left(\frac{1}{3}\right)^2}$$

$$I_{A2} = 1,05 \text{ A}$$

$$U_V = -RI_{A2} = -E = -(15 + j5) = (-15 - j5) \text{ V}$$

$$U_V = |U_V| = \sqrt{(-15)^2 + (-5)^2}$$

$$U_V = 15,81 \text{ V}$$


c)

$$S_E = EI_{A2}^* = (15 + j5) \cdot \left(1 - j\frac{1}{3}\right) = (16,67 + j0) \text{ VA}$$

$$Q_E = \text{Im}\{S_E\} = 0 \text{ VAr}$$

II-2

a)

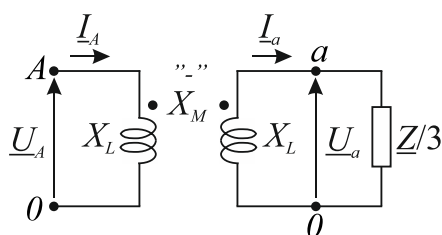

$$\underline{Z} = R - jX_C = (15 - j60) \Omega$$

$$\frac{\underline{Z}}{3} = (5 - j20) \Omega$$

$$(1) \quad \underline{U}_A = jX_L \underline{I}_A - jX_M \underline{I}_a$$

$$(2) \quad \underline{U}_a = -jX_L \underline{I}_a + jX_M \underline{I}_A$$

$$(3) \quad \underline{U}_a = \frac{\underline{Z}}{3} \underline{I}_a$$

$$(3) \Rightarrow (2) \quad -jX_L \underline{I}_a + jX_M \underline{I}_A = \frac{\underline{Z}}{3} \underline{I}_a \Rightarrow \underline{I}_a = \frac{jX_M}{\frac{\underline{Z}}{3} + jX_L} \underline{I}_A = \frac{j10}{(5 - j20) + j20} \underline{I}_A = j2 \underline{I}_A$$

$$(1) \Rightarrow \underline{U}_A = jX_L \underline{I}_A - jX_M \cdot j2 \underline{I}_A = jX_L \underline{I}_A + 2X_M \underline{I}_A$$

$$\underline{I}_A = \frac{\underline{U}_A}{jX_L + 2X_M} = \frac{230 e^{j0^\circ}}{20 + j20} = \frac{230 e^{j0^\circ}}{20\sqrt{2} e^{j45^\circ}}$$

$$\underline{I}_A = 8,13 e^{-j45^\circ} A$$

$$\underline{I}_B = 8,13 e^{-j165^\circ} A$$

$$\underline{I}_C = 8,13 e^{-j285^\circ} A$$

$$\underline{I}_a = j2 \underline{I}_A = 2 e^{j90^\circ} \cdot 8,13 e^{-j45^\circ}$$

$$\underline{I}_a = 16,26 e^{j45^\circ} A$$

$$\underline{I}_b = 16,26 e^{-j75^\circ} A$$

$$\underline{I}_c = 16,26 e^{-j195^\circ} A$$

b)

$$I_{amp} = |\underline{I}_A| = 8,13 A$$

$$U_V = |\underline{U}_{BC}| = \sqrt{3} |\underline{U}_A| = \sqrt{3} \cdot 230 = 398,4 V$$

$$P_W = \operatorname{Re}\{\underline{U}_{B0} \underline{I}_B^*\} = \operatorname{Re}\{\underline{U}_B \underline{I}_B^*\} = U_B I_B \cos \angle(\underline{U}_B, \underline{I}_B) = U_A I_A \cos(165^\circ - 120^\circ) = 230 \cdot 8,13 \cdot \cos 45^\circ$$

$$P_W = 1322,22 W$$

c)

